

15:44

30413

Problema 2

ALU ctrl Function

1000

And

0001

Or

0011

Xnor

0110


Add

1110

Subtract

1100

Multiply by 2 (ALUout = 2A)

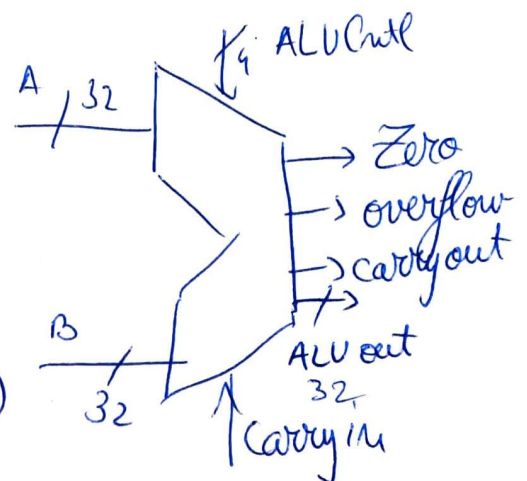

library IEEE;

use IEEE.std_logic_1164.all;

use IEEE.std_logic_arith.all;

use IEEE.std_logic_unsigned.all;

~~entity ALU is~~

~~port (A, B: in std_logic_vector(31 down to 0);~~

~~ALUout: out std_logic_vector(31 down to 0);~~

~~end ALU;~~

architecture arch of ALU is

~~begin~~

entity ALU is

port (A, B: in std_logic_vector(31 downto 0);

ALUctrl: in std_logic_vector(3 downto 0);

Carryin: in std_logic;

Zero, overflow, carryout: out std_logic;

ALUout: out std_logic_vector(31 downto 0));

end ALU;

Architecture arch of ALU is
signal = extended: ^{A[31] B[31] carry} std-logic - vector (32 downto 0);
begin

process (A, B, ALUcntl)

begin

Case ALUcntl is

when "0000" =>

-- and

~~ALUout <= A and B;~~

ALUout <= A and B;

Zero <= '0';

overflow <= '0';

Carryout <= '0';

when "0001" =>

-- or

ALUout <= A or B;

Zero <= '0';

overflow <= '0';

Carryout <= '0';

when "0011" =>

-- xor

ALUout <= A xor B;

Zero <= '0';

overflow <= '0';

Carryout <= '0';

when "1100" =>

-- multiply-by-2

ALUout <= A(30 downto 0) & '0'; -- shift left

If A < "100...0" then

^{31 bits}
overflow <= '0';

else
overflow <= '1';

end if;

if A = "00...0" ^{32 bits} then

Zero <= '1';

else

Zero <= '0';

end if;

carryout \leftarrow '0';
 when "0110" \Rightarrow -- add
 ~~$A1 \leftarrow$ '0' & $A(31 \text{ downto } 0)$;~~
 ~~$B1 \leftarrow$ '0' & $B(31 \text{ downto } 0)$;~~
 ~~$\text{extended} \leftarrow A1 + B1$;~~
 ~~$\text{ALU out} \leftarrow \text{extended}(31 \text{ downto } 0)$;~~
 ~~$\text{carryout} \leftarrow \text{extended}(32)$;~~
~~if $\text{extended}(31 \text{ downto } 0) = \underbrace{"000 \dots 0"}_{32 \text{ bits}}$ then~~
 ~~$\text{zero} \leftarrow$ '1';~~
~~else~~
 ~~$\text{zero} \leftarrow$ '0';~~
~~endif;~~
 ~~$\text{overflow} \leftarrow \text{extended}(32)$;~~ -- in this situation I
 -- considered overflow and
 -- carryout to be the same

when "1110" \Rightarrow -- subtract $A - B$

if $A < B$ then
 $\text{carryout} \leftarrow$ '1';

else
 $\text{carryout} \leftarrow$ '0';

end if;
 $\text{overflow} \leftarrow$ '0';

if $A = B$ then
 $\text{zero} \leftarrow$ '1';

else
 $\text{zero} \leftarrow$ '0';

end if;
 $A1 \leftarrow$ '0' & $A(31 \text{ downto } 0)$;

$B1 \leftarrow$ '0' & $B(31 \text{ downto } 0)$;

$\text{extended} \leftarrow A1 - B1$;

$\text{ALU out} \leftarrow \text{extended}(31 \text{ downto } 0)$;

when others \Rightarrow
 ALU out

When "0110" \Rightarrow -- add

$A1 \leftarrow '0' \& A(31 \text{ downto } 0);$

$B1 \leftarrow '0' \& B(31 \text{ downto } 0);$

$\text{carryEx} \leftarrow \underbrace{"00 \dots 0"}_{32 \text{ bits}} \& \text{carryIn};$

$\text{extended} \leftarrow A1 + B1 + \text{carryEx};$

$\text{ALUout} \leftarrow \text{extended}(31 \text{ downto } 0);$

$\text{Carryout} \leftarrow \text{extended}(32);$

$\text{overflow} \leftarrow \text{extended}(32);$

if $\text{extended}(31 \text{ downto } 0) = \underbrace{"00 \dots 0"}_{32 \text{ bits}}$ then

$\text{zero} \leftarrow '1';$

else

$\text{zero} \leftarrow '0';$

end if;

-- I considered OF and carry
-- to represent the same

when others \Rightarrow

$\text{zero} \leftarrow '0';$

$\text{overflow} \leftarrow '0';$

$\text{Carryout} \leftarrow '0';$

$\text{ALUout} \leftarrow \underbrace{"0'0 \dots 0"}_{32 \text{ bits}};$

end case;

end process;

end arch;