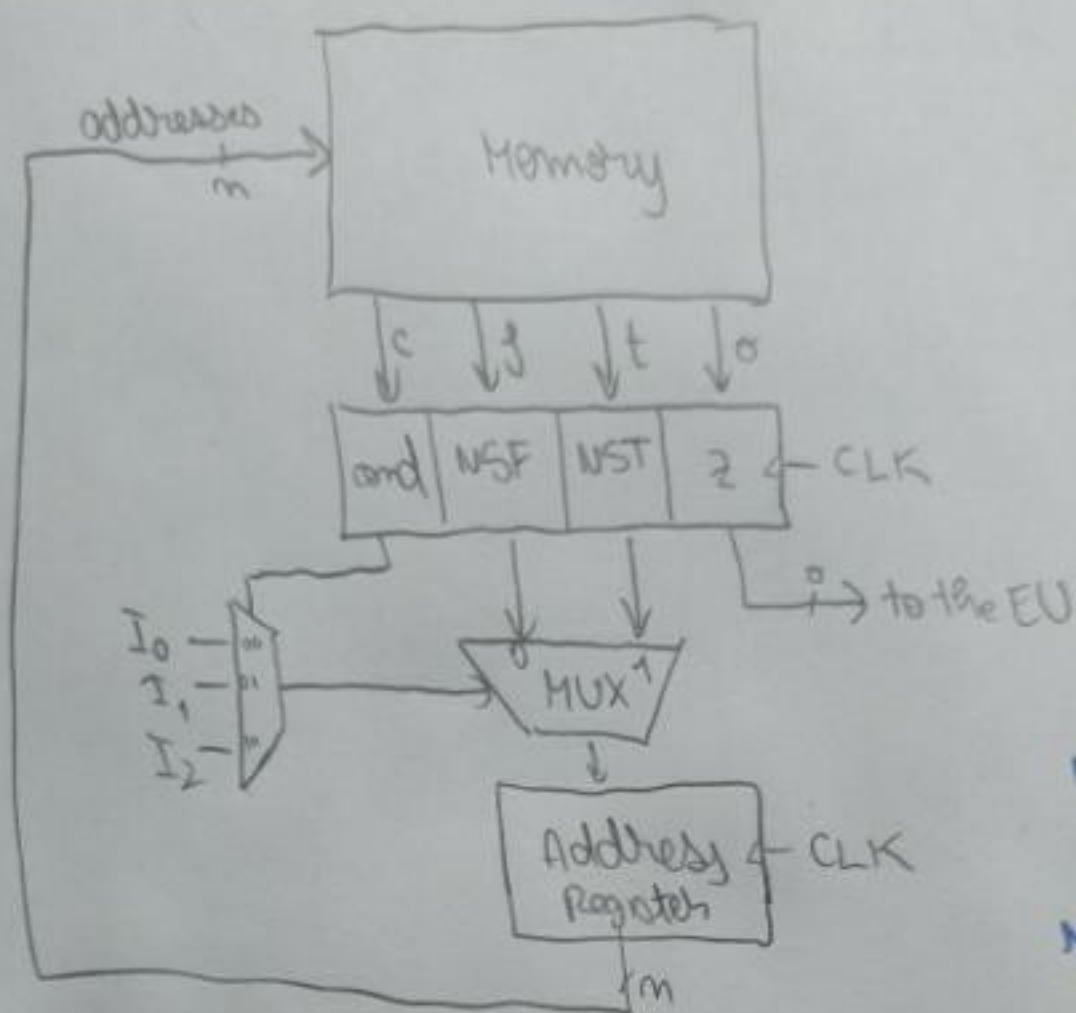


5. We create

- a) The implementation is done with state addressing with pair addresses, because the outputs only depend on the current state, so this is a Mealy machine.



All inputs have 0 on the left and 1 on the right

NSF = next state if false
NST = next state if true

We have: 3 inputs so condition is on 2 bits, $C=2$
3 states so we encode them on 3 bits

$$\Rightarrow m = f = t = 3$$

3 outputs ~~we encode~~ \Rightarrow 3 bits, $\theta = 3$

b) The necessary memory capacity is

$$2^m (C + f + t + o) = 2^3 (2 + 3 + 3 + 3) = 2^3 \cdot 11$$

a) We continue the implementation

cond	
00	I_0
01	I_1
10	I_2
11	X

States encoding: Standby: 0000 000
Run: 001
Suspend: 010
Resume: 011
Wait: 100

Memory Map:

Address	cond	NSFalse	NSTrue	Outputs		
				z1	z2	z3
Standby 000	00	000	001	1	1	0
Run 001	01	010	001	0	1	1
Suspend 010	XX	011	011	1	0	0
Resume 011	01	001	100	0	0	0
Wait 100	10	100	000	1	1	0
101	XX	XX	XX	X	X	X
110	XX	XX	XX	X	X	X
111	XX	XX	XX	X	X	X

c) Standby: A, Run: B, Suspend: C, Resume: D, Wait: E

I States	0	1
A	A/110	B/110
B	C/011	B/011
C	D/100	D/100
D	B/000	E/000
E	E/110	A/110

Each state only has 1 input,

Do we consider that

one on the columns
for simpler
representation

d) The only possible compatible equivalent states are A and E because they have the same output, that would mean A has to be equivalent with E and A with B, which isn't possible

So the automaton's no. of states can't be reduced;