 


# **TRANSFER BETWEEN REGISTERS and THREE STATE LOGIC**


# Introduction

- Bus design is made using **Three State Logic**, implemented at circuit outputs
- For information transfer, usually are used three state registers, three state bus amplifiers (uni or bi directional), together with decoders
- Important examples will follow

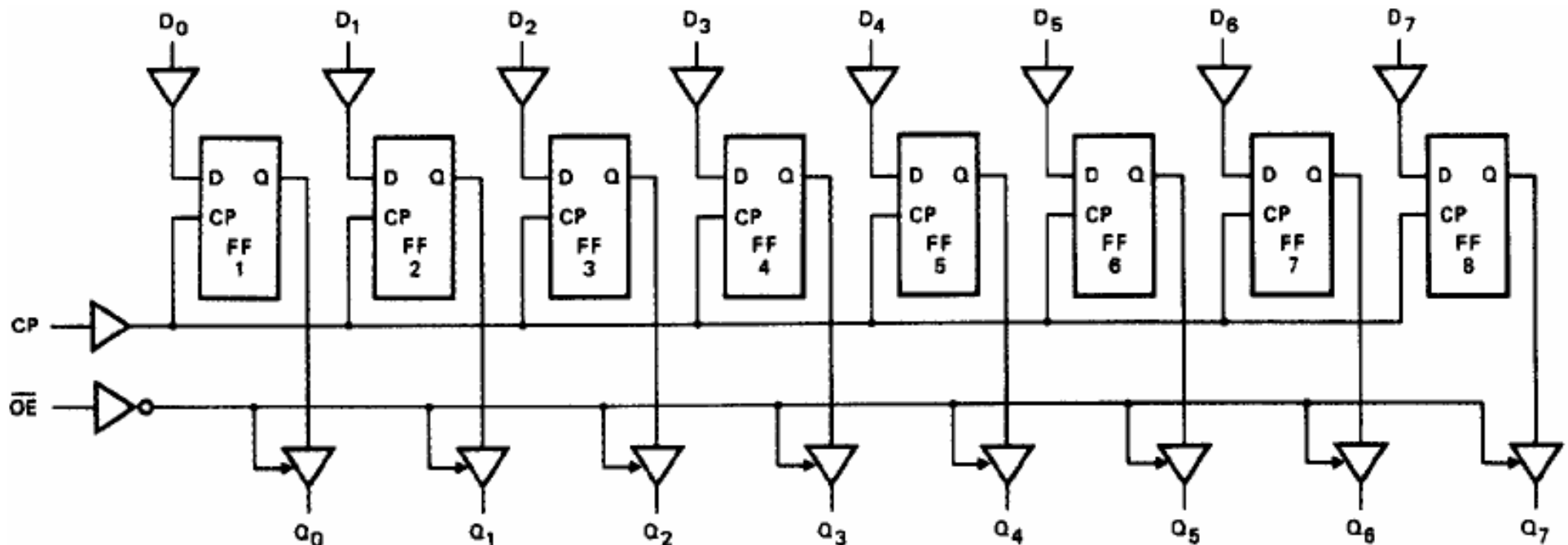
# 74374 REGISTER




- 8 D type flip flops, outputs are buffered with three state circuits, activated using Output Enable command signal  $\overline{OE}$  (signal is effective on '0' logic); so, output data will be available if signal  $\overline{OE}$  is Low
- Writing data into register is made on the positive front of clock signal CP



# 74373 Register


 


 - 8 D type flip-flops, with outputs buffered with three-state circuits, enabled with OE\ input, zero-active
- Data are sent at outputs while LE input is '1'.
- When LE goes '0' data are stored in latches.



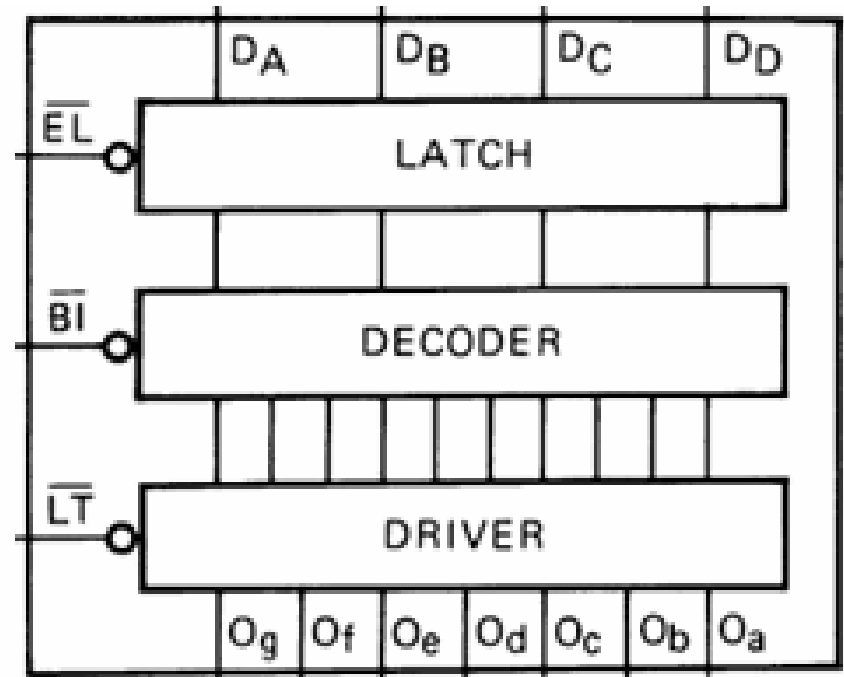 
# 4511 - latch, decoder, driver

- Control of 7-segments LED display
- Functions: latch, decoder BCD to 7 segments and driver
- 4 data inputs ( $D_A$ - $D_D$ )
- 1 latch enable input, '0' active ( $\overline{EL}$ )
- 1 blanking input (all segments off), '0' active ( $\overline{BI}$ )
- 1 test lamp input (all segments on), '0' active ( $\overline{LT}$ )
- 7 outputs for segments, '1' active ( $O_a$ - $O_g$ )





 
- When  $\overline{EL}$  is '0',  $O_a$ - $O_g$  are imposed by  $D_A$ - $D_D$
- When  $\overline{EL}$  is '1', last values for  $D_A$ - $D_D$  are latched and  $O_a$ - $O_g$  present steady values
- If  $\overline{LT}$  is '0',  $O_a$ - $O_g$  are '1' no matter input values



- If  $\overline{LT}$  is '1', '0' value for  $\overline{BI}$  drives  $O_a$ - $O_g$  into '0'
- If  $\overline{LT}$  and  $\overline{BI}$  are '1', outputs  $O_a$ - $O_g$  present values depending on decoder



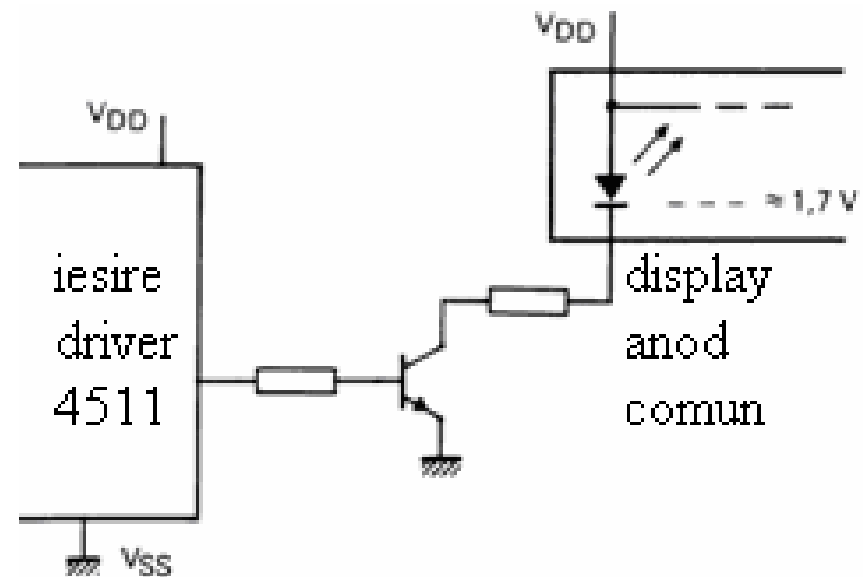 
 
- For having a high value for the output current, the output circuit is a bipolar transistor
- Output voltage depends on the generated current
- For  $V_{DD}=5V$ :
- $I_{OH}=0mA \rightarrow V_{OHmin}=4,10V, V_{OHtyp}=4,40V$
- $I_{OH}=10mA \rightarrow V_{OHmin}=3,60V, V_{OHtyp}=4,25V$
- $I_{OH}=20mA \rightarrow V_{OHmin}=2,80V, V_{OHtyp}=4,20V$





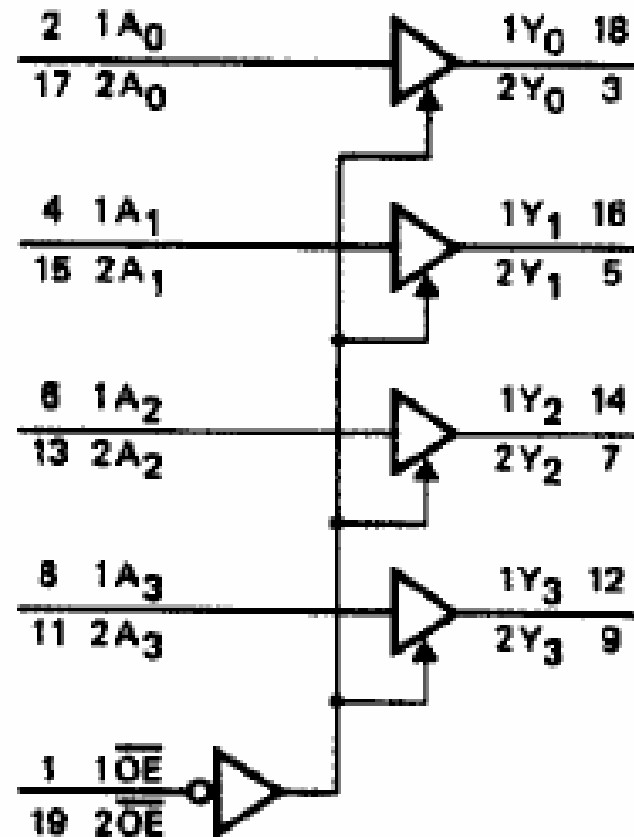
 
# Unidirectional Amplifier 74244

- 8 three state amplifiers, outputs are effective if enable signals  $1\overline{OE}$  and  $2\overline{OE}$  are Low
- The two enable input signals allow to activate independently each set of 4 outputs: outputs  $1Y_0 - 1Y_3$  will be enabled by low active signal  $1\overline{OE}$  and outputs  $2Y_0 - 2Y_3$  will be enabled by signal  $2\overline{OE}$


  
# Bidirectional Amplifier 74245



- 16 three state amplifiers, eight for each direction
- Logic state for DIRECTION input signal DIR allows selecting group of eight amplifiers whose outputs may be activated (enabled) : DIR='1' data sent from inputs  $A_i$  to outputs  $B_i$ , DIR='0' data sent from inputs  $B_i$  to outputs  $A_i$
- $\overline{OE}$ ='1' disables all outputs,  $\overline{OE}$ ='0' enables outputs selected by signal DIR


  
## Decoder 74138

3 address inputs, 8 Low active outputs and  
3 enable signals

If  $E1 \neq '0'$ ,  $E2 \neq '0'$  si  $E3 = '1'$  output  $Y_i$  selected by  
binary combination of address signals  $A0$ ,  $A1$  &  
 $A2$ , will be '0', the rest of outputs being '1'




For any other combination of  
values for enable inputs  $E1$ ,  
 $E2$  &  $E3$ , all outputs will be '1'

For disabled circuit, all outputs  
will NOT be in HZ state, but in  
logic '1'; this way, the low  
active outputs will NOT select  
other circuits
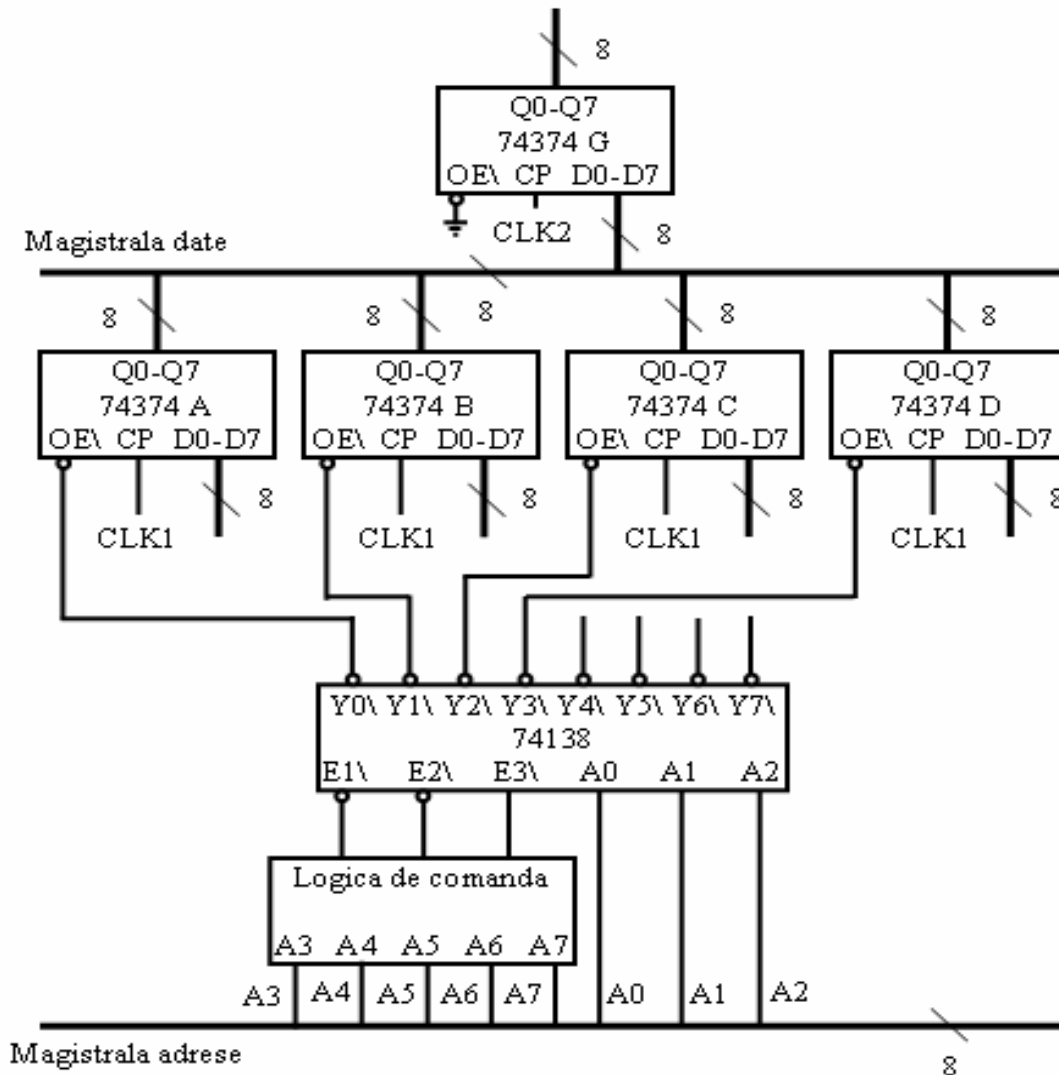
# TRANSFER BETWEEN REGISTERS (1)

Data from one (out of four registers: A, B, C or D), is transferred in a fifth one, G

Common data bus (8 lines), either output data from registers A, B, C or D, either input data for register G



Activating one register: a result of decoding some address lines from the address bus; corresponding active Output Enable line (OE\ ) will select register

For selecting a register all address lines are considered (total selection)


Advantage – all address space may be used

Drawback – selection circuit complex

Data writing made on raising edges of the clock signals CLK1 & CLK2

Register G is selected all time

## REGISTER TRANSFER (2)

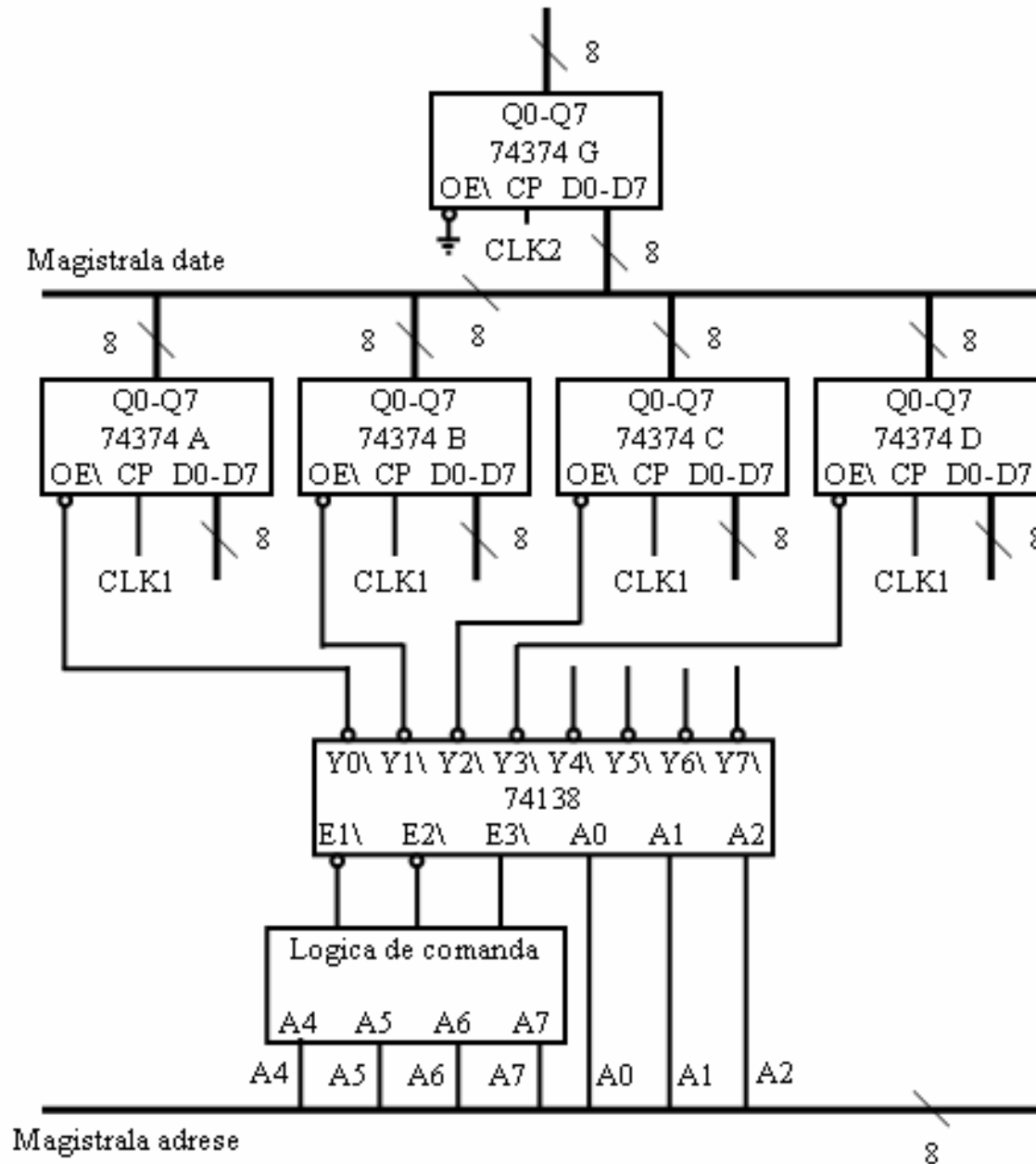

For partial selection method, only a part of address space is used

Advantage – lower complexity


Drawback – fewer selection possibilities

## REGISTER TRANSFER (3)

Linear selection method: only one address line used for selection


Advantage – minimum complexity

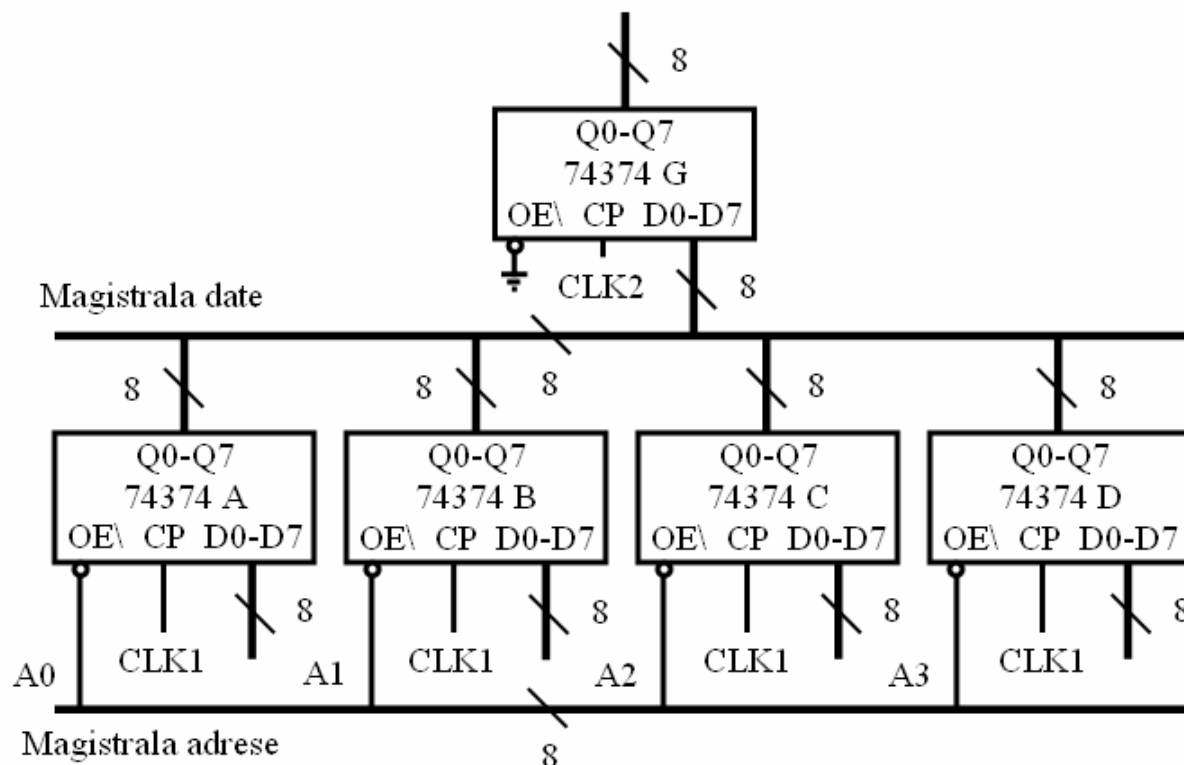Drawback – very few possibilities for selecting within a more complex circuit


 
# Proposed Problems

- Design an un-adapted transmission line with 5 OpenCollector transmitters and 5 TTL standard receivers.



$$R_{1\max} = \frac{V_{CC\min} - V_{OH\min}}{5I_{OH} + 5I_{IH}} \approx 1,6k\Omega$$

$$R_{1\min} = \frac{V_{CC\max} - V_{OL\max}}{I_{OL} + 4I_{OH} - 5I_{IL}} \approx 0,5k\Omega$$

$$R_1 = 1k\Omega$$

- Design an adapted line with 10 OC transmitters and 2 TTL standard receivers. Bus line has a characteristic impedance of  $Z_0 = 250\Omega$ .

$$R_{1\max} = \frac{V_{CC\min} - V_{OH\min}}{10 I_{OH} + 2 I_{IH}} \approx 910\Omega$$

$$R_{1\min} = \frac{V_{CC\max} - V_{OL\max}}{I_{OL} + 9 I_{OH} - 2 I_{IL}} \approx 322\Omega$$

$$R_1 = 330\Omega$$

$$Z_0 = \frac{R_1 R_2}{R_1 + R_2}; R_2 = \frac{Z_0 R_1}{R_1 - Z_0} \approx 1k\Omega$$

$$V_{OH} = \frac{V_{CC\min} R_2}{R_1 + R_2} \approx 3,5V$$

