

Analog measuring instruments

Classical Electrical Measurements

- **Indicating analog meters**
- **Analog Meters-Classifications and Symbols.**
- **Types of analog instruments.**
 - Moving Coil Instruments
 - Moving Iron Instruments
 - Electrodynamic Instruments
- **Voltmeters. Ammeters, Wattmeters, Ohmmeters**
- **Measurements with Bridges**
 - Wheatstone Bridge. Principle. Applications
 - The Balanced and the Unbalanced DC Bridges
 - Stress, Strain, and Strain Gages
 - Types of AC bridges


Indicating analog meters

- A **pointer** is moving along a graduated scale
- **Continuous** varying readout
- Easy to track changes in meter reading
- Analog multimeters are sometimes referred to as "**volt-ohm-meters**", abbreviated **VOM**.
- They are simple, reliable and they have low price
- Indicating instruments:
 - Electromechanical type
 - Electronic type



Analog meters. Classifications and symbols

Analog meter panel

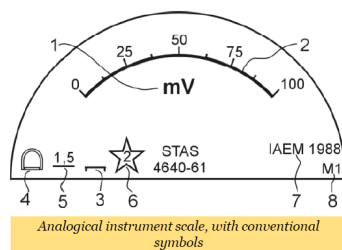

1. The parameter to be measured (voltage, current...)
2. The scale (linear, square, logarithmic)
3. Scale position



vertical




horizontal



inclined


Analog meter panel

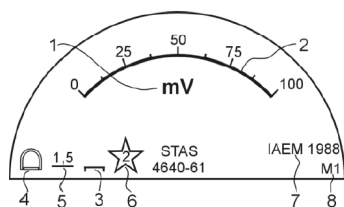

Analogical instrument scale, with conventional symbols


4. Conventional symbol of the instrument

	Permanent-magnet moving-coil instrument		Vibrating-reed instrument
	Permanent-magnet ratiometer		(*) Non-insulated thermocouple (thermal converter)
	Moving permanent-magnet instrument		(*) Insulated thermocouple (thermal converter)
	Moving permanent-magnet ratiometer		(*) Electronic device in a measuring circuit
	Moving-iron instrument		(*) Rectifier
	Polarized moving-iron instrument		Shunt
	Moving-iron ratiometer		Series resistor
	Ironless electrodynamic instrument		Electric screen
	Iron-cored electrodynamic (ferro-dynamic) instrument		Magnetic screen
	Ironless electro-dynamic ratiometer		Astatic instrument
	Iron-cored electrodynamic (ferro-dynamic) ratiometer		Earth (ground) terminal (general symbol)
	Induction instrument		Zero (span) adjuster

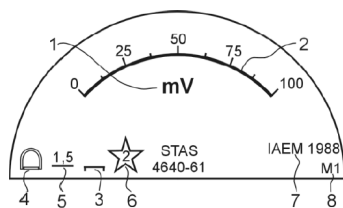

Analogical instrument scale, with conventional symbols

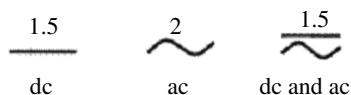5. Class of accuracy and the nature of measured quantity



6. Testing voltage for electric insulation –kV (Instrument safety)

	Test voltage 500 V
	Test voltage above 500 V (e.g. 2 kV)
	Apparatus not subjected to a voltage test

Analog meters principles

x- measured quantity (electrical energy)

a- pointer deflection (mechanical energy)

$$\boxed{x} \xrightarrow{\text{force}} F \xrightarrow{\text{torque}} M_d \xrightarrow[\text{M}_r]{\text{balance}} M_d + M_r = 0 \rightarrow \alpha$$


$$M_d - \text{Deflecting Torque} \begin{cases} M_d = f(x) \\ M_d = f(x, \alpha) \end{cases}$$

$$M_r - \text{Controlling (restoring) Torque} \begin{cases} \text{Spring control} \\ \text{Gravity control} \end{cases}$$


Spring control- is twisted in opposite direction

$$M_r = -D\alpha$$

D – specific restoring torque

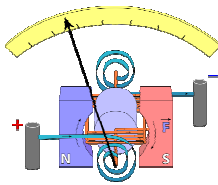

Gravity control

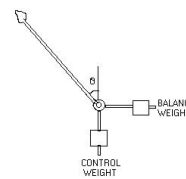

When the moving system **is in motion** there are also:

$$M_{da} - \text{Damping Torque} \quad M_{da} = -F \frac{d\alpha}{dt}$$

- F- is the specific damping torque
- The pointer comes to its final position without overshooting

M_f — Friction Torque

$$M_f = k_f G^n$$

k_f —friction coefficient
G- movement weight


M_J — Inertia Torque

$$M_J = -J \frac{d^2 \alpha}{dt^2}$$

J-moment of inertia

The general equation of the moving mechanism in dynamic conditions:
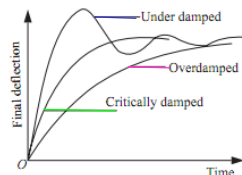
$$M_d + M_r \pm M_f + M_J + M_{da} = 0 \quad J \frac{d^2 \alpha}{dt^2} + F \frac{d\alpha}{dt} + D\alpha \pm M_f = f(x, \alpha)$$



The balance condition will be:

$$M_d + M_r = 0$$



Types of analog instruments

Permanent-magnet moving-coil (PMMC) instrument

$$M_d = k_d \cdot I \quad \text{DC-direct current} \quad K_d\text{-dynamic constant}$$

$$k_d = NBS \begin{cases} \rightarrow \text{N-number of wire} \\ \rightarrow \text{B-induction} \\ \rightarrow \text{S-coil area} \end{cases}$$

$$M_r = -D\alpha$$

$$M_d + M_r = 0 \Leftrightarrow k_d I - D\alpha = 0$$

The permanent deflection will be:


$$\alpha_p = \frac{k_d}{D} \cdot I$$

The sensitivity of this instrument:


$$S_I = \frac{d\alpha}{dI} = \frac{k_d}{D}$$

Finally: $\alpha_p = S_I \cdot I \rightarrow$ This instrument type has a **linear scale**

These instruments work only in d.c !!!

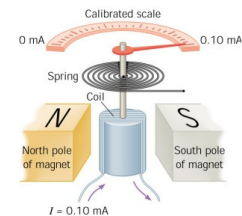


α -angle of rotation

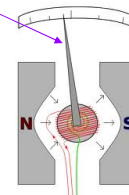



Moving coil instruments with rectifiers

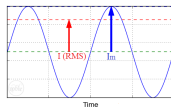Considering a PMMC instrument connected to an **AC (alternative current)** power supply :



$$i = I_m \sin \omega t = I\sqrt{2} \sin \omega t$$

$$I = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

RMS (root mean square)

The instantaneous torque is:



$$m_d = k_d i$$

The **average (mean)** torque for a full period will be **zero**:



$$M_{d \text{ average}} = \frac{1}{T} \int_0^T m_d dt = \frac{1}{T} k_d \int_0^T I_m \sin \omega t dt = 0$$

The solution is the **rectifier** instrument.

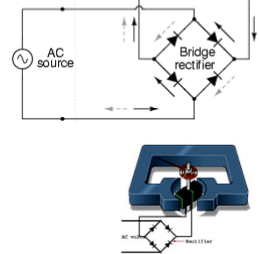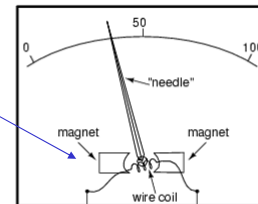meter displays the **average value** of the input waveform



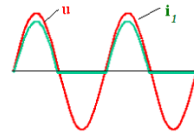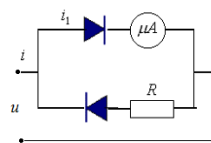Moving-coil instrument with **half-wave rectifier (1)**



The **average rectified value (arv)** of the current that flows through the instrument coil is:

$$I_{arv1} = \frac{1}{T} \int_0^T i_1 dt$$

where

$$i_1 = \begin{cases} \sqrt{2}I \sin \omega t, & \dots t \in \left[0, \frac{\pi}{2}\right] \\ 0 & \dots t \in \left[\frac{\pi}{2}, \pi\right] \end{cases}$$


Half wave rectified (1)

$$I_{arv1} = \frac{\sqrt{2}}{\pi} I = \frac{1}{2,22} I$$

The permanent deflection will be:

$$\alpha_p = S_I I_{arv1} = \frac{S_I}{2,22} I$$

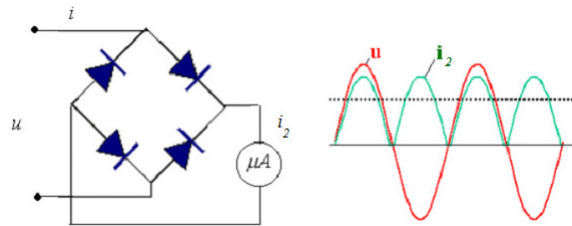Moving-coil instrument with **full-wave rectifier**



The **average rectified value (arv)** of the current that flows through the instrument coil is:

$$I_{avr2} = \frac{1}{T} \int_0^T i_2 dt = \frac{1}{T} \int_0^T |i| dt = \frac{1}{T} \int_0^T \sqrt{2} I |\sin \alpha| dt = 2 \frac{\sqrt{2}}{\pi} I = \frac{1}{1.11} I$$

Full wave rectified (2)

$$I_{avr2} = \frac{1}{1.11} I$$

The permanent deflection will be: $\alpha_p = \frac{S_I}{1.11} I$

Meters are often calibrated to directly display **r.m.s.** of sinusoidal waves !!!

The **form factor** of sinusoidal current is:

$$k_f = \frac{\text{rms value}}{\text{arv value}} \quad k_{f \sin} = \frac{I_{rms}}{I_{avr2}} = \frac{I}{\frac{1}{1.11} I} = 1.11 \quad \Rightarrow \quad k_{f \sin} = 1.11$$

The instruments are often calibrated in **rms (effective values) I** of **sinusoidal wave** ($k_{f \sin}$), so we read:






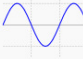
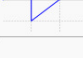
$$I_{read} = I_{k_{f \sin} = 1.11} \longrightarrow \text{r.m.s for 1.11}$$

If we measure another waveform (another form factor k'_f) the result must be adjusted in with a correction factor:

$$\text{correction factor} = \frac{k'_f}{1.11}$$

$$I' = \frac{k'_f}{1.11} \cdot I_{read}$$

Form Factors-Different waveforms

Waveform	Image	RMS	ARV	Form Factor
Sine wave		$\frac{a}{\sqrt{2}}$	$\frac{2}{a-\pi}$	$\frac{\pi}{2\sqrt{2}} \approx 1.11072073$
Half-wave rectified sine		$\frac{a}{2}$	$\frac{a}{\pi}$	$\frac{\pi}{2} \approx 1.5707963$
Full-wave rectified sine		$\frac{a}{\sqrt{2}}$	$\frac{2}{a-\pi}$	$\frac{\pi}{2\sqrt{2}}$
Square wave, constant value		a	a	$\frac{a}{a} = 1$
Pulse wave $D = \frac{\tau}{T}$ duty cycle		$a\sqrt{D}$	aD	$\frac{1}{\sqrt{D}} = \sqrt{\frac{T}{\tau}}$
Triangle wave		$\frac{a}{\sqrt{3}}$	$\frac{a}{2}$	$\frac{2}{\sqrt{3}} \approx 1.15470054$
Sawtooth wave		$\frac{a}{\sqrt{3}}$	$\frac{a}{2}$	$\frac{2}{\sqrt{3}}$
Gaussian white noise $U(-1,1)$		$\frac{1}{\sqrt{3}}$	$\frac{1}{2}$	$\frac{2}{\sqrt{3}}$

84

Application: Measuring non-sinusoidal waveforms

The voltage waveform shown in the figure is applied to an AC voltmeter (PMMC instrument with full wave rectifier). The instrument is calibrated to measure voltages with sinusoidal waveform.

- a) Find the **form factor** of the measured waveform
 b) Find the voltage that is **read** on the instrument and find the **correction factor**

$$a) \quad k_{f_{\text{saw-tooth}}} = \frac{V_{\text{rms}}}{V_{\text{avr 2}}}$$


$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v_1^2(t) dt} = \sqrt{\frac{1}{2} \int_{-1}^1 (50t)^2 dt} = \sqrt{\frac{1}{2} \cdot 2500 \cdot \frac{t^3}{3} \Big|_{-1}^1} = \sqrt{\frac{1}{2} \cdot 2500 \cdot \frac{1+1}{3}} = \frac{50}{\sqrt{3}} [V]$$

$$V_{\text{avr 2}} = \frac{1}{T} \int_0^T |v_1(t)| dt = \frac{1}{2} \cdot \frac{2 \cdot 50}{2} = 25 [V]$$


Aria of triangle

$$k_{f_{\text{saw-tooth}}} = \frac{\frac{50}{\sqrt{3}}}{25} = \frac{2}{\sqrt{3}} = 1.154$$
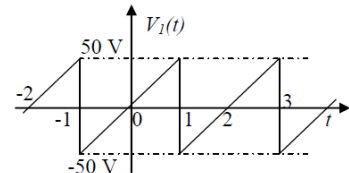
$$b) \quad V_{\text{read}} = V_{\text{avr 2}} \cdot k_{f_{\text{sin}}} = 25 \cdot 1.11 = 27.75 [V]$$


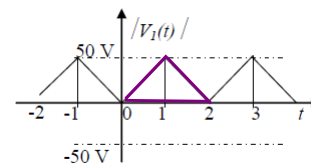
$$\left. \begin{aligned} v_1(t) &= At + B \\ -50 &= -A + B \\ 50 &= A + B \end{aligned} \right\} \Rightarrow A = 50, B = 0 \Rightarrow v_1(t) = 50t$$



$$\text{correction factor} = \frac{k'_f}{1.11} = \frac{1.154}{1.11} = 1.04$$

Moving-iron instrument (in ac and dc)

They can be of two types:

- **With attraction:** the soft iron vane is drawn into the field
- **With repulsion:** double iron instrument

They measure a.c. signals at frequencies up to 125 Hz.

The deflecting torque $M_d = \frac{1}{2} \frac{dL}{d\alpha} I^2$

$\frac{dL}{d\alpha}$ → is the rate of change of the inductance of coil with the rotation of moving iron

I → is the effective value of ac through the coil


$$M_d + M_r = 0$$

$$\frac{1}{2} \frac{dL}{d\alpha} I^2 - D\alpha = 0$$

$$\alpha_p = \frac{1}{2D} \frac{dL}{d\alpha} I^2$$

Nonlinear scale

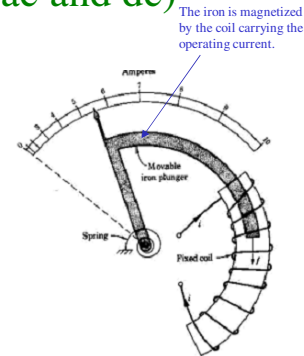These instruments are used in industrial applications (c=1; 2; 2,5)






Attraction type



Electrodynamic instruments


The most accurate indicating instruments

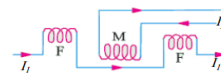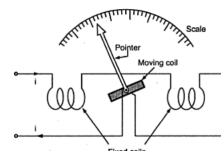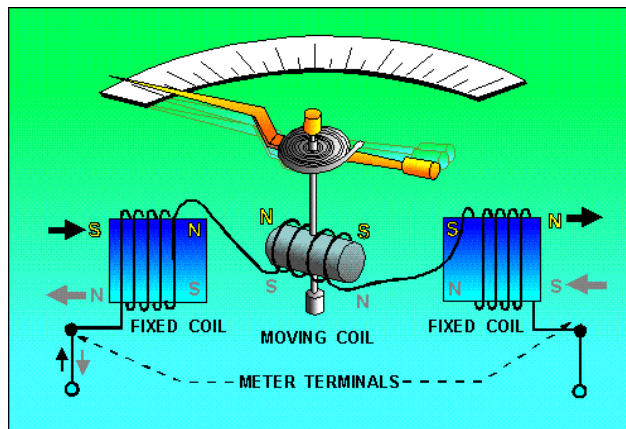

They measure both d.c. signals and a.c. signals up to a frequency of 2 kHz

They are **transfer-type instruments**.

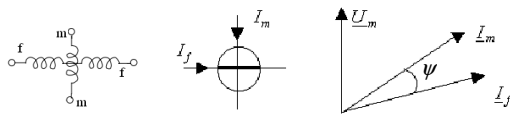A transfer instrument is one that may be calibrated with a d.c. source and then used without modification to measure a.c.



The deflecting torque

$$M_d = \frac{dM}{d\alpha} I_f I_m \cos \psi \quad (AC)$$

$$M_d = \frac{dM}{d\alpha} I_f I_m \quad (DC)$$

M is the mutual inductance between the fixed coil and moving coil.


If the restoring torque is $M_r = -D\alpha$ then the permanent deflection of these kind of instruments will be:

$$\alpha_p = \frac{1}{D} \frac{dM}{d\alpha} I_f I_m \cos \psi \quad (AC)$$

$$\alpha_p = \frac{1}{D} \frac{dM}{d\alpha} I_f I_m \quad (DC)$$

These kind of instruments have a high accuracy ($c=0,05$). They are used like standard instruments. In ac they can be used until 500-1000Hz. They are sensitive to the influence of external magnetic fields, so they have an astatic construction.

Electrodynamic voltmeter

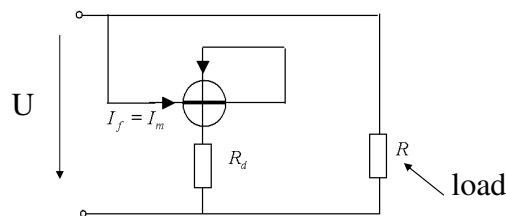

$$I_m = I_f = \frac{U}{R_v}$$

The total resistance R_v of the measuring circuit


$$R_v = R_m + R_f + R_d$$

- R_m is the resistance of moving coil
- R_f is the resistance of fixed coil
- R_d is the dropping resistor


The permanent deflection will be

In d.c. $\rightarrow \alpha_p = \frac{1}{D} I_m I_f \frac{dM}{d\alpha} = \frac{1}{D} \frac{U^2}{R_v^2} \frac{dM}{d\alpha} = f(U^2)$ In a.c. $\rightarrow \alpha_p = f'(U^2)$

Electrodynamic ammeter

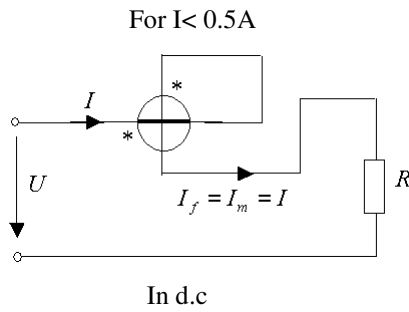

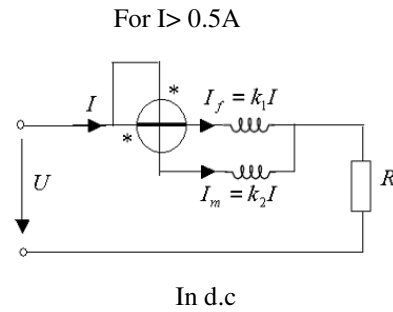
$$\alpha_p = \frac{1}{D} I_m I_f \frac{dM}{d\alpha} = \frac{1}{D} I^2 \frac{dM}{d\alpha} = f(I^2)$$



$$\alpha_p = \frac{1}{D} I_m I_f \frac{dM}{d\alpha} = \frac{k_1 k_2}{D} I^2 \frac{dM}{d\alpha} = f(I^2)$$

Electrodynamic wattmeter

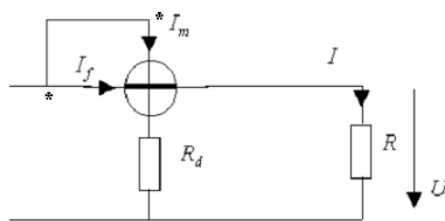

$$I_f = I$$


$$I_m = \frac{U}{R_m + R_d}$$

$$\frac{dM}{d\alpha} = k \quad (\text{Through a proper design})$$


In d.c $\longrightarrow \alpha_p = \frac{1}{D} k \frac{U}{R_m + R_d} I = K' P$

In a.c $\longrightarrow \alpha_p = \frac{1}{D} k \frac{U}{R_m + R_d} I \cos \psi = K' P$

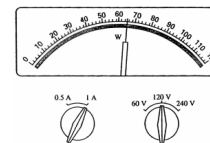The wattmeter constant $\longrightarrow C_w = \frac{U_n I_n}{\alpha_{\max}}$



Wattmeter connection

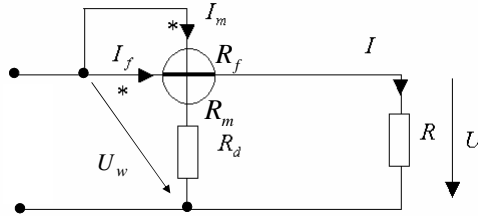

Upstream

$$P_R = UI$$

$$U = U_w - R_f I_f$$

$$I = I_f$$

$$P_R = (U_w - R_f I_f) I_f = P_w - R_f I_f^2$$

$$P_R = P_w - R_f I^2$$


$$P_R = P_w - R_f I^2$$

$$P_R = P_w - R_f \left(\frac{U}{R} \right)^2$$

$$P_R \approx P_w$$

→ For medium and high resistance values (R)

Wattmeter connection

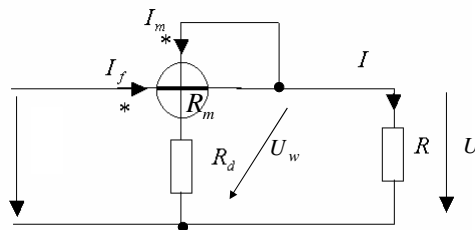

Downstream

$$P_R = UI$$

$$U = U_w$$

$$I = I_f - I_m = I_f - \frac{U_w}{R_d + R_m}$$

$$P_R = U_w \left(I_f - \frac{U_w}{R_d + R_m} \right)$$

$$P_R = U_w I_f - U_w \frac{U_w}{R_d + R_m}$$

$$P_R = P_w - \frac{U^2}{R_m + R_d}$$

$$P_R = P_w - \frac{(RI)^2}{R_m + R_d}$$

$$P_R \approx P_w$$

→ For low resistance values (R)


Voltmeters, ammeters, ohmmeters

Voltmeter...voltage measurement...parallel connection


Ammeter...current measurement...series connection

Ammeter shunt

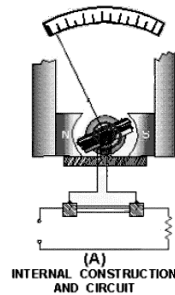A shunt is a **low-resistance conductor connected in parallel (shunt) with the meter terminals**. It is used to carry the majority of the load current.



Internal shunts
External shunts

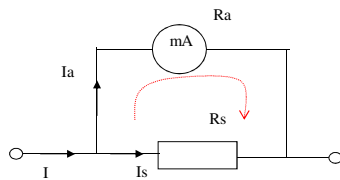

$$R_a I_a = R_s I_s \Rightarrow R_s = \frac{R_a I_a}{I_s}$$

$$I = I_a + I_s, \Rightarrow I_s = I - I_a$$


$$R_s = \frac{I_a R_a}{I - I_a} \Rightarrow R_s = \frac{R_a}{\frac{I}{I_a} - 1}$$

The multiplying power of the shunt:


$$n = \frac{I}{I_a}$$

The value of the shunt will be:

$$R_s = \frac{R_a}{n - 1}$$

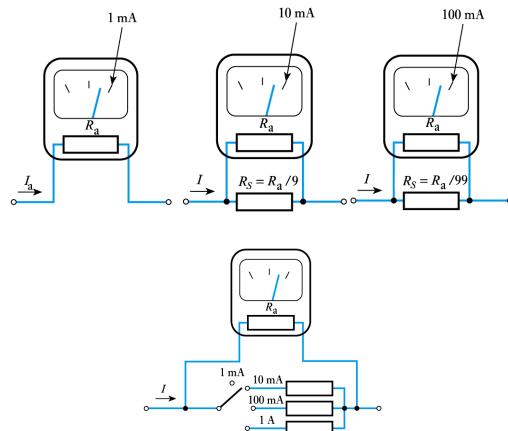

Ammeter shunt

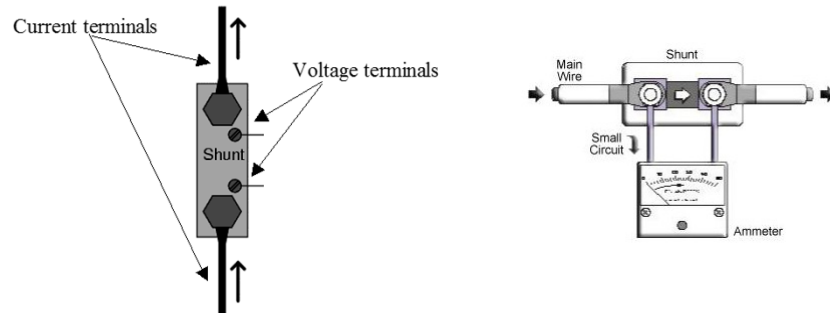

- The shunt resistor's resistance: $\text{m}\Omega$ or $\mu\Omega \rightarrow$
- Resistance this low is comparable to wire connection resistance, which means voltage measured across such a shunt must be done so in such a way as to avoid detecting voltage dropped across wire connections \rightarrow
- Shunts are usually equipped with four connection terminals

Voltmeter sensitivity

The diagram shows a voltmeter symbol (a circle with 'V') with current I_V flowing through it and resistance R_V . A voltage U_{max} is indicated across the voltmeter.


$$S_V = \frac{1}{I_V} = \frac{1}{\text{full-scale current}}$$

$$S_V = \frac{R_V}{U_{\text{max}}} \quad [S_V] = \frac{\Omega}{V}$$

$$R_V = S_V \cdot U_{\text{max}}$$

Specific resistance \rightarrow R_V \leftarrow On the scale \rightarrow

Voltmeter dropping resistor

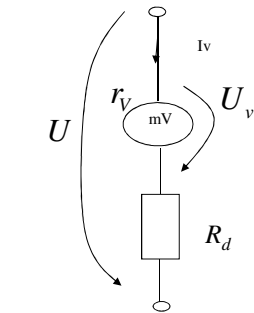

$$U = R_d I_v + U_v$$


$$U = R_d \frac{U_v}{r_v} + U_v$$

$$U = U_v \left(\frac{R_d}{r_v} + 1 \right) \Rightarrow R_d = r_v \left(\frac{U}{U_v} - 1 \right)$$

Multiplying power

$$m = \frac{U}{U_v}$$


$$R_d = r_v (m - 1)$$

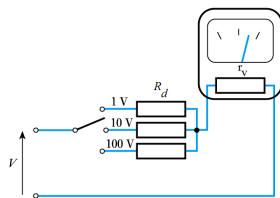

Analog ohmmeter

An **ohmmeter** is normally part of a **volt-ohm-milliammeter (VOM)**. Ohmmeters do not usually exist as individual instruments.

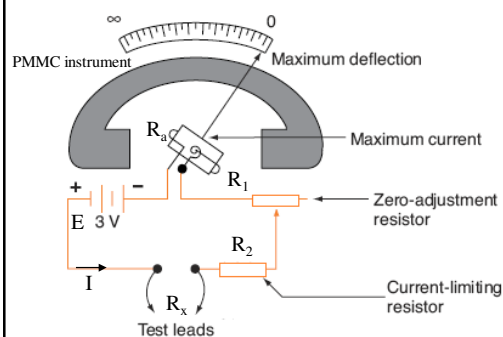
Series ohmmeter: for measuring low values of R_x (10^2 - $10^5 \Omega$)



$$I = \frac{E}{R_a + R_1 + R_2 + R_x}$$

Short circuit
If $R_x = 0 \Rightarrow I_{\max} = \frac{E}{R_a + R_1 + R_2}$

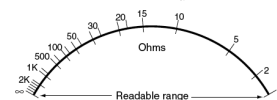Open break
If $R_x = \infty \Rightarrow I_{\min} = \lim_{R_x \rightarrow \infty} \frac{E}{R_a + R_1 + R_2} = 0$



Inverse and non linear scale!!!

Parallel ohmmeter (Shunt type ohmmeter): for measuring **very low** values of R_x (10^{-1} - $10^2 \Omega$)

The megohmmeter ($M\Omega$)(Megger): for measuring **very high** resistance \rightarrow to test the insulation found in power transmission systems, electrical machinery, transformers and so on.

Application : Series ohmmeter

A series ohmmeter is made up of a $E=1.5$ V battery, a low-current PMMC instrument and $R_a+R_1+R_2=15k\Omega$.

(a) Determine the current in the instrument when $R_x=0$.

(b) Determine how the resistance scale should be marked at 0.5 FS, 0.25 FS, and 0.75 FS. (FS-Full Scale)

(a)
$$I = \frac{E}{R_a + R_1 + R_2 + R_x} = \frac{1.5}{15 \cdot 10^3} = 100 \mu A$$


(b) At 0.5FS $\longrightarrow I_{0.5FS} = \frac{100 \mu A}{2} = 50 \mu A \longrightarrow \frac{E}{R_a + R_1 + R_2 + R_{x1}} = I_{0.5FS}$

$$R_a + R_1 + R_2 + R_{x1} = \frac{E}{I_{0.5FS}} = \frac{1.5}{50 \cdot 10^{-6}} = 30 k\Omega$$

$$15 k\Omega + R_{x1} = 30 k\Omega \Rightarrow R_{x1} = 15 k\Omega$$

At 0.25FS $\longrightarrow I_{0.25FS} = \frac{100 \mu A}{4} = 25 \mu A \longrightarrow R_{x2} = 45 k\Omega$

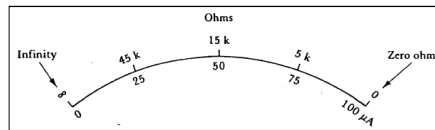At 0.75FS $\longrightarrow I_{0.75FS} = 3 \frac{100 \mu A}{4} = 75 \mu A \longrightarrow R_{x3} = 5 k\Omega$




Measurements with Bridges


DC&AC Bridges

Measurements with Bridges

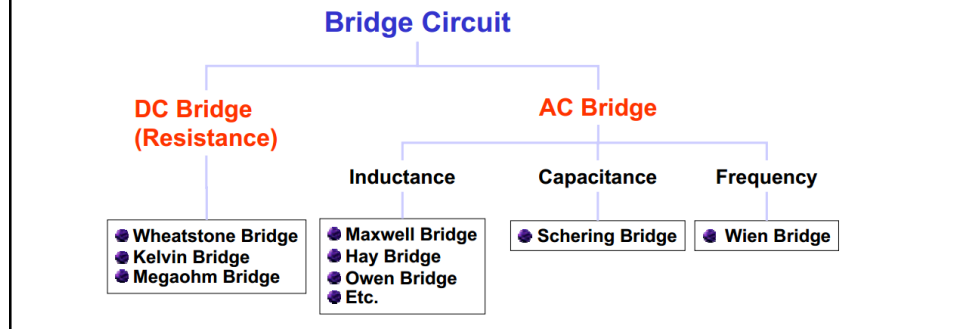- Bridges use the null measurement method (comparison principle).
- A known (standard) value is adjusted until it is equal to the unknown value.



The balanced DC Wheatstone Bridge

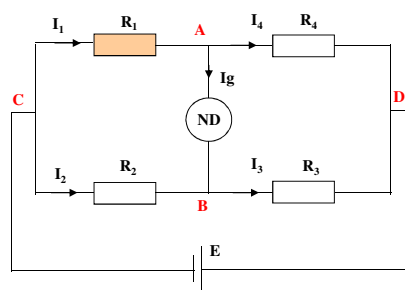

- $R_x = R_1$; R_x - the unknown resistor (range of 1–10⁶Ω)
- R_4 - a calibrated variable resistance
- R_2 and R_3 - fixed known resistors
- ND - Null Detector-Galvanometer (PMMC type sensitive ammeter)

Balance condition:

$$U_{AB} = 0 \quad (I_g = 0)$$


No potential difference across the galvanometer (no current through the galvanometer)

$$U_{AB} = 0 \Leftrightarrow U_{AC} = U_{BC} \Leftrightarrow R_1 \cdot I_1 = R_2 \cdot I_2 \quad (a)$$

$$U_{AB} = 0 \Leftrightarrow U_{AD} = U_{BD} \Leftrightarrow R_4 \cdot I_4 = R_3 \cdot I_3 \quad (b)$$

But: $I_g = 0 \Leftrightarrow I_1 = I_4 \quad I_2 = I_3$

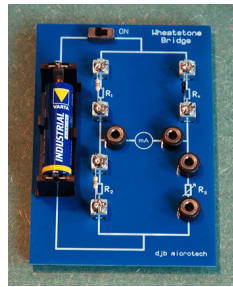It results: $(a)/(b) \Leftrightarrow \frac{R_1}{R_4} = \frac{R_2}{R_3} \Rightarrow R_1 \cdot R_3 = R_2 \cdot R_4$



$$R_1 \cdot R_3 = R_2 \cdot R_4$$

The unknown resistor will be:

$$R_x = R_1 = \frac{R_2}{R_3} R_4$$

$\frac{R_2}{R_3}$ \longrightarrow is the *measure ratio* and it gives the order of R_x

R_4 \longrightarrow is the *adjustable resistance* (fine adjustments)

Application: Wheatstone Bridge


Consider using a Wheatstone bridge having $R_2 = 2000 \, \Omega$ and $R_3 = 200 \, \Omega$ to measure a resistance, R_1 , of a temperature sensor. Suppose the resistance of the temperature sensor, $R_1[\Omega]$, is related to the temperature $T[^\circ\text{C}]$, by the equation

$$R_1 = 1500 + 25T$$


The bridge is balanced by adjusting R_4 until $R_4 = 250 \, \Omega$. What is the value of the temperature?

$$R_1 = \frac{R_2}{R_3} R_4 = \frac{2000 \cdot 250}{200} = 2500 \, \Omega$$
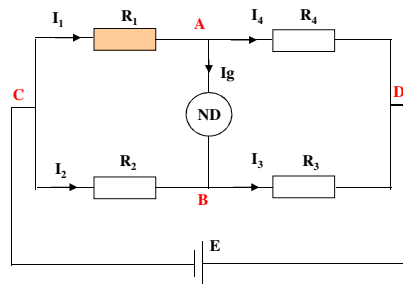
$$T = \frac{R_1 - 1500}{25} = \frac{2500 - 1500}{25} = 40^\circ\text{C}$$




The Wheatstone bridge sensitivity

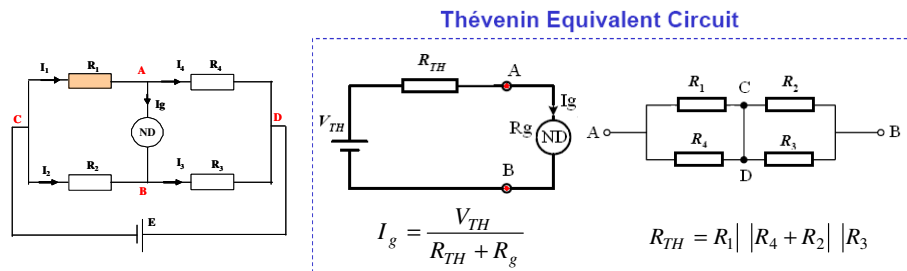

The permanent deflection of the ND (galvanometer):

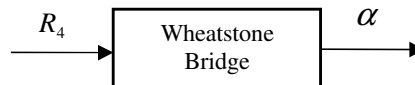
$$\alpha_p = S_I I_g = S_I E \frac{R_2 R_4 - R_1 R_3}{A R_4 + B} \text{ where } A = f_1(R_1, R_2, R_3, R_g); B = f_2(R_1, R_2, R_3, R_g)$$




The absolute sensitivity:

$$S = \lim_{\Delta R_4 \rightarrow 0} \frac{\Delta \alpha}{\Delta R_4} = S_I E \frac{R_2}{A R_4 + B}$$

The Wheatstone bridge sensitivity


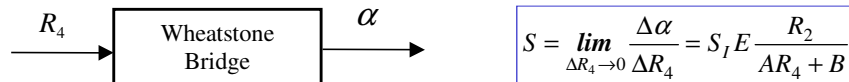

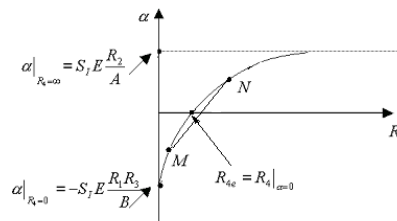
$$S = \lim_{\Delta R_4 \rightarrow 0} \frac{\Delta \alpha}{\Delta R_4} = S_I E \frac{R_2}{A R_4 + B}$$



- Bridge sensitivity increases with S_I and with E . The value of **E is limited** because the currents in the bridge branches are limited.
- Bridge sensitivity tends to zero when $R_4 = \infty$. \Rightarrow
- **Wheatstone bridge** is used to measure **medium values of resistances**.
- **Kelvin Bridge** is used to measure **small values** of resistances (0.00001 to 1 Ω)
- **Megaohm Bridge** is used to measure **high values** of resistances (10^6 to 10^{12} Ω)


The unbalanced Wheatstone bridge

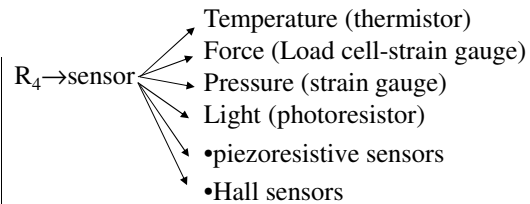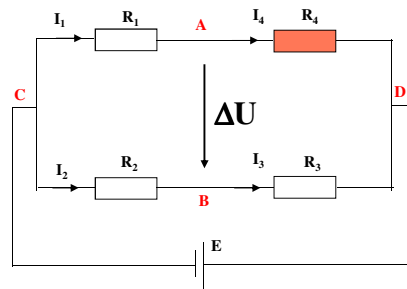

Initially $\Delta U = 0$ ($R_1 R_3 = R_2 R_4$) \longrightarrow Balanced bridge


$R_4 \rightarrow R_4 + \Delta R$ \longrightarrow $\Delta U \neq 0$ \longrightarrow Unbalanced bridge

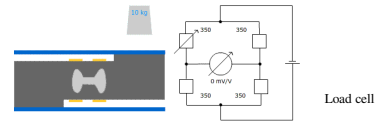The amount of ΔU is the amount of parameter being measured.
 ΔU must be amplified!!!



Stress, Strain and strain gages

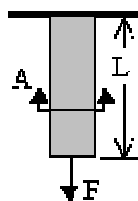We consider a wire or cylinder, fixed at the top, and hanging down. A force F is applied.




A - original cross sectional area

L -original wire length

The material will experience a stress, called **axial stress**.

$$\sigma_a = \frac{F}{A} \quad [\sigma_a] = \frac{N}{m^2} \longrightarrow \text{pressure}$$

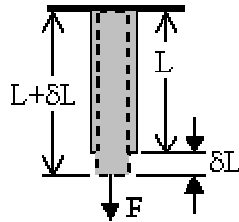
When F increases then L increases and A decreases.



Axial strain (deformation)

$$\epsilon_a = \frac{\delta L}{L} \quad (\text{nondimensional})$$

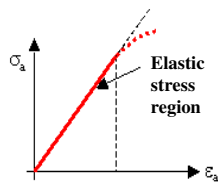The Hooke's law: For elastic materials \rightarrow stress is proportional to strain.



$$\sigma_a = E \epsilon_a$$

$E \rightarrow$ Young's modulus (modulus of elasticity)
For a given material is a constant.

The electrical resistance R of a wire:

$$R = \frac{\rho L}{A}$$

We apply logarithm:

$$\ln R = \ln \rho + \ln L - \ln A$$

By differentiating:

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \frac{dA}{A}$$


It is demonstrated that:

$$\frac{dR}{R} = S \frac{dL}{L}$$

- The resistance of the wire increases with deformation
- S-strain gauge factor (sensitivity)
- Usually **S=2** (2-6 metals, 40-200 semiconductors)
- The strain and stress can be measured

Displacement, acceleration, pressure, temperature, liquid level, stress, force or torque can be determined using **strain measurements**.

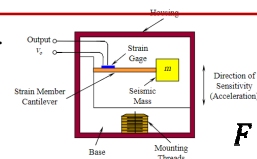- A cantilever beam fixed to the housing of the instrument.
- A mass is fixed to the free end of the cantilever beam.
- Two bonded strain gauges are mounted on the cantilever beam
- Damping is provided by a viscous fluid filled inside the housing.




$$F = ma$$


A strain gauge accelerometer

Strain gauges

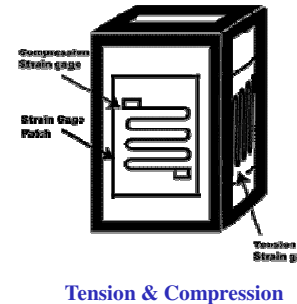- Strain gauges are measuring elements that convert force, pressure, tension, etc., into an electrical signal.
- A strain gauge is a resistive elastic sensor whose resistance is a function of **applied strain** (unit **deformation**).
- A Wheatstone bridge converts this change in resistance to an absolute voltage.
- Most strain gauges are smaller than a postage stamp.



Strain gauges

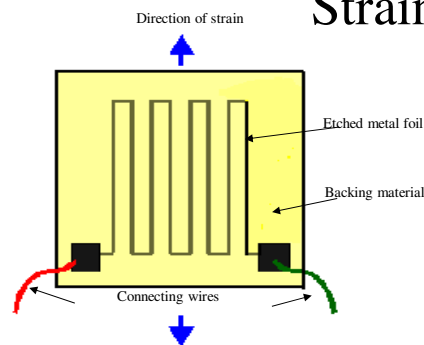

Typically $R=120\Omega$ or 350Ω

- A **strain gauge** consists of a **small diameter** wire (actually an etched **metal foil**), which is attached to a **backing material** (usually plastic).
- The wire **is looped** back and forth several times to create an **effectively longer wire**. The longer the wire, the larger the resistance, and the larger the change in resistance with strain.


gravat

How are strain gauges used?

- Sustained beam \rightarrow axial strain
- The strain must be measured.
- A strain gauge is glued to the surface of the beam.

$$\frac{dR}{R} = S \frac{dL}{L}$$

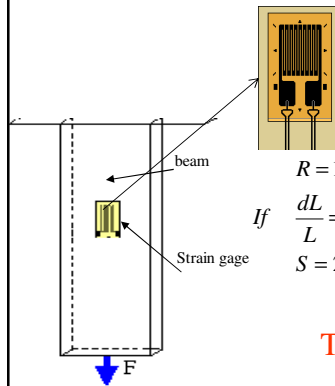- S is the gauge factor
- R is the nominal resistance of the gauge
- dR is the change in resistance due to the strain.



$$R = 120 \, \Omega$$


$$\text{If } \frac{dL}{L} = 10^{-6} \dots 10^{-3} \quad S = 2$$

$$\Rightarrow dR = RS \frac{dL}{L} = 0,00024 \Omega \dots 0,24 \Omega \quad \leftarrow \text{VERY SMALL}$$

The ohmmeter can not measure it!

SOLUTION: The Unbalanced Wheatstone Bridge

The unbalanced Wheatstone bridge

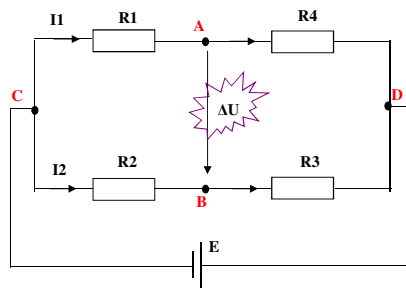

$$\Delta U = V_A - V_B = V_A - V_D - (V_B - V_D) = U_{AD} - U_{BD}$$


$$U_{AD} = E \frac{R_4}{R_1 + R_4}$$

$$U_{BD} = E \frac{R_3}{R_2 + R_3}$$

$$\Delta U = E \left(\frac{R_4}{R_1 + R_4} - \frac{R_3}{R_2 + R_3} \right) = E \frac{R_2 R_4 + R_3 R_4 - R_1 R_3 - R_4 R_3}{(R_1 + R_4)(R_2 + R_3)}$$

$$\Delta U = E \frac{R_2 R_4 - R_1 R_3}{(R_1 + R_4)(R_2 + R_3)}$$

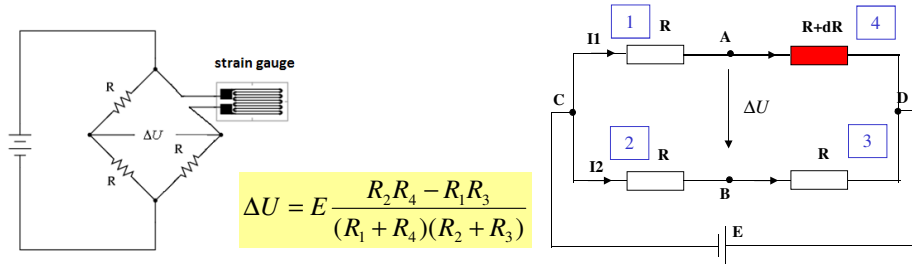The unbalanced Bridge with a **single** strain gauge (Quarter Bridge)



$$\Delta U = E \frac{R_2 R_4 - R_1 R_3}{(R_1 + R_4)(R_2 + R_3)}$$

Considering the bridge *with equal arms* then $R_1 = R_2 = R_3 = R$

$$\Delta U = E \frac{R(R+dR) - RR}{(R+R+dR)(R+R)} = E \frac{RdR}{(2R+dR)2R}$$

$$\Delta U = E \frac{dR}{(2R+dR)2} \approx E \frac{dR}{4R} \Rightarrow \frac{dR}{R} = 4 \frac{\Delta U}{E}$$

$$\frac{dR}{R} = S \frac{dL}{L} \Leftrightarrow \frac{dL}{L} = \frac{1}{S} \frac{dR}{R}$$


Linear response

Bridge sensitivity

$$S_r = \frac{\Delta U / E}{dR / R} = \frac{1}{4}$$

$$\frac{dL}{L} = \frac{1}{S} 4 \frac{\Delta U}{E}$$

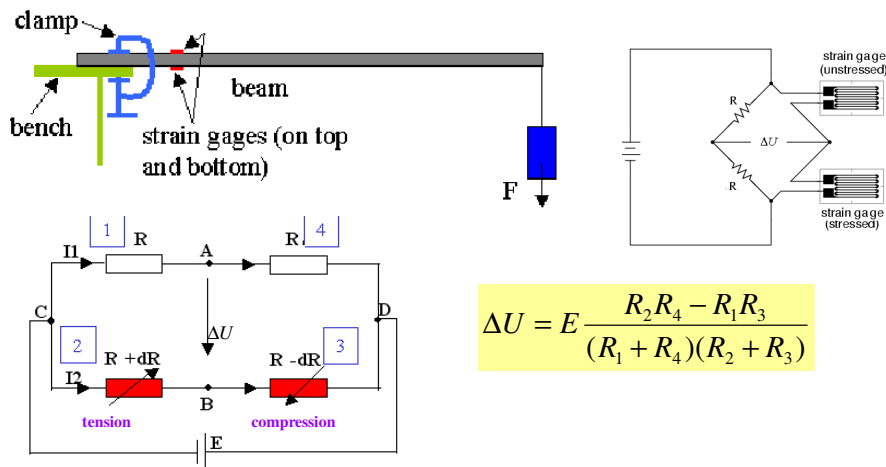The Unbalanced Bridge with **two** strain gauges (half bridge)



$$\Delta U = E \frac{R_2 R_4 - R_1 R_3}{(R_1 + R_4)(R_2 + R_3)}$$

$$\Delta U = E \frac{(R+dR)R - R(R-dR)}{2R2R} = E \frac{2RdR}{2R2R} = \frac{E}{2R} dR$$

If sensor 1 and sensor 2 are exposed to the pressure but they are exposed to the same temperature variation, is the output changing?

Half bridge






Bridge sensitivity

$$S_r = \frac{\Delta U / E}{dR / R} = \frac{1}{2}$$



$$\frac{dL}{L} = \frac{1}{S} 2 \frac{\Delta U}{E}$$

Linear response

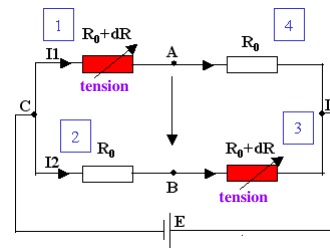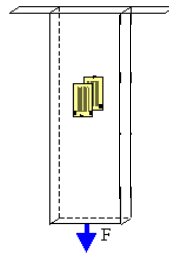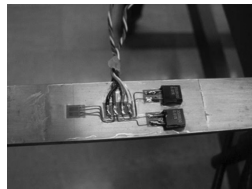The same result is obtained in the next situation:



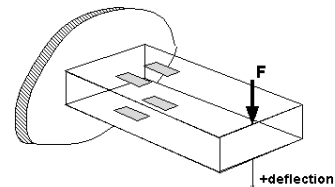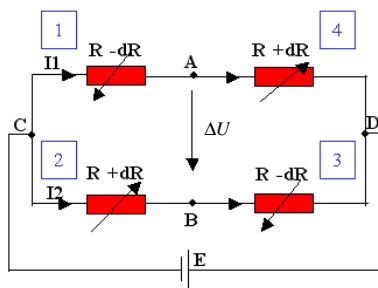The Unbalanced Bridge with four strain gauges (full bridge)



$$\Delta U = E \frac{R_2 R_4 - R_1 R_3}{(R_1 + R_4)(R_2 + R_3)}$$


$$\Delta U = E \frac{(R + dR)^2 - (R - dR)^2}{2R2R} = E \frac{2R2dR}{2R2R} = \frac{E}{R} dR$$

Bridge sensitivity

$$S_r = \frac{\Delta U / E}{dR / R} = 1$$

$$\frac{dL}{L} = \frac{1}{S} \frac{\Delta U}{E}$$

Linear response

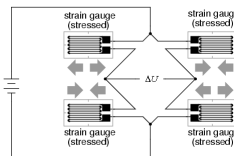


Two force sensors suitable for a bathroom scale, each containing a pair of strain gauges that will flex oppositely under load

AC Bridges (Impedance Bridges)

They are used to measure: inductance L, capacitance C, storage factor (quality factor), loss factor, frequency of audio signals

They can be used also a oscillator circuits

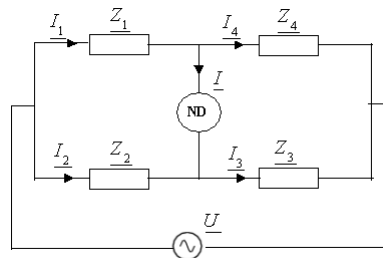- signal generators
- to determine an unknown circuit parameter by measuring the oscillating frequency



$$\underline{Z}_1 = Z_1 e^{j\varphi_1}$$

$$\underline{Z}_2 = Z_2 e^{j\varphi_2}$$

$$\underline{Z}_3 = Z_3 e^{j\varphi_3}$$

$$\underline{Z}_4 = Z_4 e^{j\varphi_4}$$

ND-null detector-headphone; vibration galvanometer

The ac source is an oscillator of $f=40\dots 125\text{Hz}$

The balance condition $\underline{I} = 0$ leads to the balance equations:

$$\begin{cases} \underline{Z}_1 \cdot \underline{I}_1 = \underline{Z}_2 \cdot \underline{I}_2 \\ \underline{Z}_4 \cdot \underline{I}_4 = \underline{Z}_3 \cdot \underline{I}_3 \\ \underline{I}_1 = \underline{I}_4; \quad \underline{I}_2 = \underline{I}_3; \end{cases} \Leftrightarrow \frac{\underline{Z}_1}{\underline{Z}_4} = \frac{\underline{Z}_2}{\underline{Z}_3} \Leftrightarrow \underline{Z}_1 \cdot \underline{Z}_3 = \underline{Z}_2 \cdot \underline{Z}_4$$

$$\underline{Z}_1 \underline{Z}_3 e^{j(\varphi_1 + \varphi_3)} = \underline{Z}_2 \underline{Z}_4 e^{j(\varphi_2 + \varphi_4)} \quad (\text{polar form})$$

The balance condition will be:

$$\begin{cases} \underline{Z}_1 \cdot \underline{Z}_3 = \underline{Z}_2 \cdot \underline{Z}_4 & \text{magnitude condition} \\ \varphi_1 + \varphi_3 = \varphi_2 + \varphi_4 & \text{phase condition} \end{cases}$$

$$(\underline{R}_1 + j\underline{X}_1) \cdot (\underline{R}_3 + j\underline{X}_3) = (\underline{R}_2 + j\underline{X}_2) \cdot (\underline{R}_4 + j\underline{X}_4) \Rightarrow \quad (\text{Cartesian form})$$

The balance condition will be:


$$\begin{cases} R_1 R_3 - X_1 X_3 = R_2 R_4 - X_2 X_4 \\ R_1 X_3 + R_3 X_1 = R_2 X_4 + R_4 X_2 \end{cases}$$

Remarks


$$Z_1 Z_3 e^{j(\varphi_1 + \varphi_3)} = Z_2 Z_4 e^{j(\varphi_2 + \varphi_4)}$$

If $Z_3 = R_3$; $Z_4 = R_4 \Rightarrow \varphi_3 = \varphi_4 = 0 \Rightarrow \varphi_1 = \varphi_2 \Rightarrow$

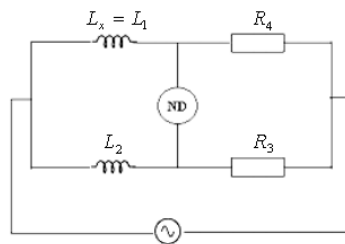\Rightarrow the others arms should contain either L_1 , L_2 or C_1 , C_2



The balance is possible

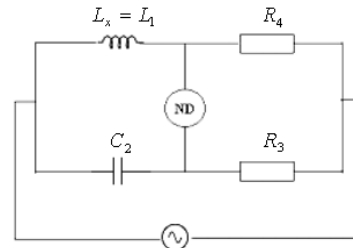


The balance is impossible

A huge number of various AC bridge circuits were designed and developed: *Maxwell, Maxwell-Wien, Wien, Schering, Hay, Owen, Anderson, de Sauty.*

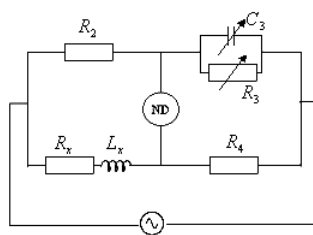Examples of ac bridges

The Maxwell-Wien bridge

For **unknown inductors**: R_x , L_x , (low Q-values inductors)



$$R_2 R_4 = (R_x + j\omega L_x) \frac{R_3 \frac{1}{j\omega C_3}}{R_3 + \frac{1}{j\omega C_3}}$$

$$R_2 R_4 = (R_x + j\omega L_x) \frac{R_3}{1 + j\omega R_3 C_3}$$

$$R_2 R_4 (1 + j\omega R_3 C_3) = R_3 (R_x + j\omega L_x)$$

$$\underbrace{R_2 R_4}_{\text{real}} + \underbrace{j\omega R_2 R_3 R_4 C_3}_{\text{imaginary}} = \underbrace{R_3 R_x}_{\text{real}} + \underbrace{j\omega L_x R_3}_{\text{imaginary}}$$

It results:

$$R_x = \frac{R_2 R_4}{R_3}$$


and

$$L_x = R_2 R_4 C_3$$

The quality factor (Q value) of the inductor will be:

$$Q = \frac{\omega L_x}{R_x} = \omega \frac{R_2 R_4 C_3}{R_2 R_4} R_3 = \omega C_3 R_3$$

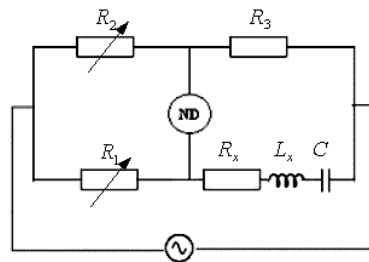The resonance bridge (for measure R, L, Q)




$$R_1 R_3 = R_2 \left(R_x + j\omega L_x + \frac{1}{j\omega C} \right)$$

$$(R_1 R_3 - R_2 R_x) j\omega C = 1 - \omega^2 L_x C$$

$$R_x = \frac{R_1 R_3}{R_2}$$

$$L_x = \frac{1}{\omega^2 C}$$

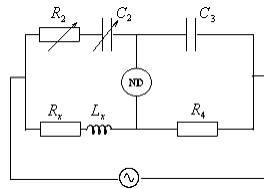The Owen bridge (for measure R, L-high values)




$$R_x = \frac{R_4 C_3}{C_2}$$

$$L_x = R_2 R_4 C_3$$

Application: Schering Bridge (for measurement of capacitors and their insulation)

A Schering bridge has the following components values: $C_1=0.1\mu\text{F}$, $R_1=2\text{k}\Omega$, $R_2=5\text{k}\Omega$, $C_3=0.25\mu\text{F}$, $f=2\text{kHz}$.

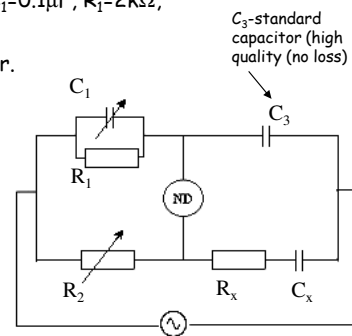Determine the unknown capacitance and dissipation factor.



$$\frac{\frac{1}{j\omega C_1} R_1}{\frac{1}{j\omega C_1} + R_1} \left(R_x + \frac{1}{j\omega C_x} \right) = R_2 \frac{1}{j\omega C_3}$$

$$\frac{R_1}{1 + R_1 j\omega C_1} \left(\frac{1 + j\omega R_x C_x}{j\omega C_x} \right) = \frac{R_2}{j\omega C_3}$$


$$\frac{R_1 (1 + j\omega R_x C_x)}{(1 + R_1 j\omega C_1) C_x} = \frac{R_2}{C_3}$$

$$R_1 C_3 (1 + j\omega R_x C_x) = R_2 C_x (1 + R_1 j\omega C_1)$$

$$R_1 C_3 = R_2 C_x \Rightarrow C_x = \frac{R_1 C_3}{R_2} = \frac{2\text{k}\Omega}{5\text{k}\Omega} \cdot 0.25\mu\text{F} = 0.1\mu\text{F}$$

$$R_x C_x = \omega R_1 C_1 \Rightarrow R_x = \frac{R_1 C_1}{C_x} = \frac{R_1 C_1}{\frac{R_1 C_3}{R_2}} = \frac{R_2 C_1}{C_3} = \frac{5 \cdot 10^3 \cdot 0.1}{0.25} = 2\text{k}\Omega$$

Dissipation factor.

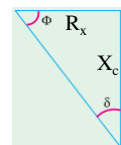

$$D = \tan \delta = \frac{R_x}{X_c} = \omega R_x C_x =$$


$$= 2\pi \cdot 2 \cdot 10^3 \cdot 2 \cdot 10^{-3} \cdot 0.1 \cdot 10^{-6} =$$

$$= 2.513$$

Application

Capacitive Pressure Sensors

$$C = \frac{\epsilon A}{d}$$

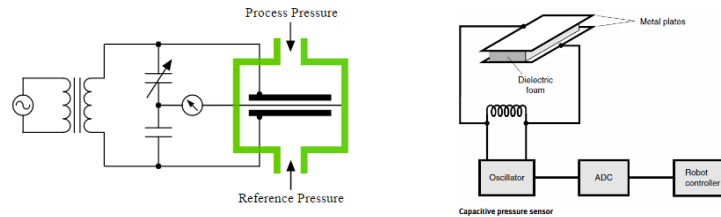


- The capacitive pressure sensors use a thin diaphragm, usually metal or metal-coated quartz, as one plate of a capacitor.
- The diaphragm is exposed to the **process pressure on one side** and to a **reference pressure on the other**. Changes in pressure cause it to deflect and change the capacitance, **that is detected by a bridge circuit.**

A capacitive pressure sensor consists of two metal plates separated by a layer of nonconductive (dielectric) foam. The resulting variable capacitor is connected in parallel with an inductor; the inductance/capacitance (LC) circuit **determines the frequency of an oscillator.**

126

Application


Inductive proximity sensors

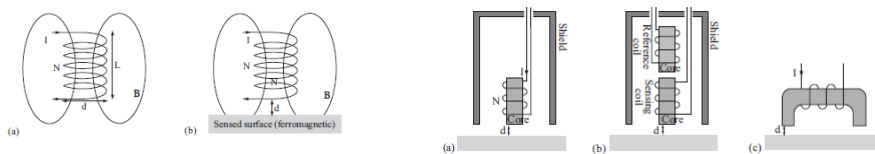

AC bridge- **measuring the inductance L**- a measure of the proximity to the surface being sensed.

Application

MEMS capacitive accelerometers

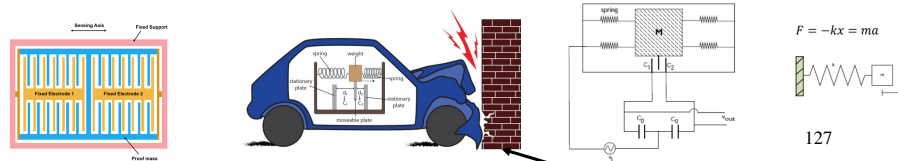

127

https://www.youtube.com/watch?v=T_iXLNkkjFo

https://www.youtube.com/watch?time_continue=7&v=RLQGZl0lpjQ

Airbag deployment