

Interfacing Sensors and Actuators

Methods and Circuits for Interfacing Sensors and Actuators

Sensors

The output is an electrical signal: U, I, R, C, L, f...

They need additional measuring circuits for:

- Amplification
 - Instrumentation amplifiers
 - Bridge Amplifiers
 - Lock-in Amplifiers
- Filtering
- Impedance matching
- Peak values detecting
- Analog to Digital conversion- for interfacing with microprocessors or digital displays

Actuators


They need high values of currents and voltages:

- Power amplifiers for driving the actuators
- Digital to Analog conversion –for interfacing with microprocessors

Other circuits:

- Excitation circuits
- Power supplies
- Oscillators

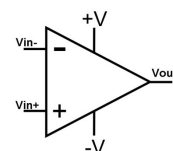
Operational
amplifiers
(Op-amp)
solutions



Amplification in instrumentation

Operational Amplifiers (OA)- Review


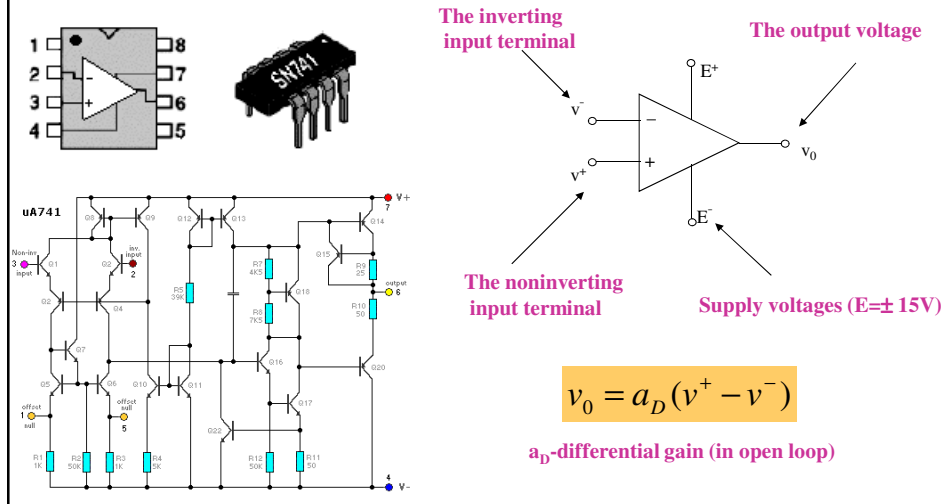
Integrated circuit that amplifies the signal across its input terminals.




Op-amps

(-) The **inverting input** terminal means:

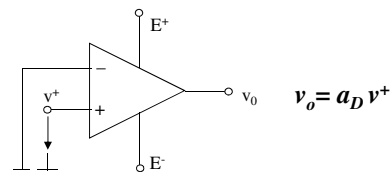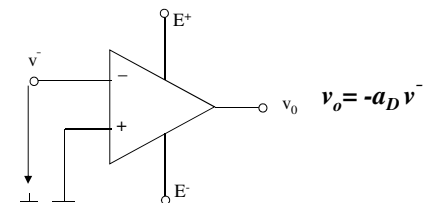(+) The **noninverting input** terminal means:



The **ideal** op-amp

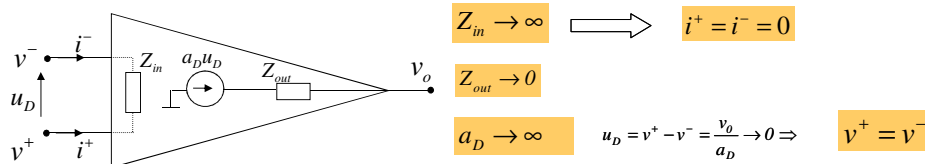


The **real** op-amp

$$Z_{in} \approx 10^6 \Omega \quad a_D \approx 10^5 - 10^9 \quad Z_{out} \approx 100 \dots 1000 \Omega$$



Offset voltage

Practically when $v^+ = v^- = 0$ the output voltage $v_o \neq 0$

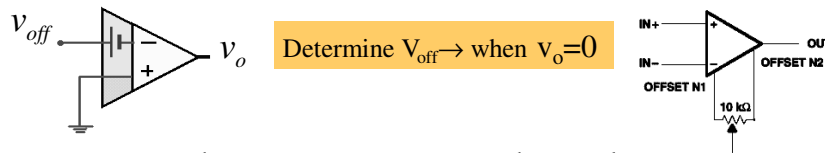Why? Because of the transistors mismatching in the input stage



The common-mode voltage

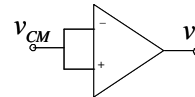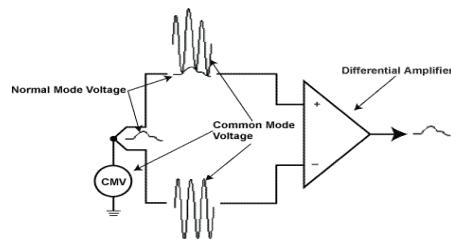

Ideally if $v_{CM} \neq 0$ then $v_o = 0$

Really if $v_{CM} \neq 0$ then $v_o = a_{CM} \cdot v_{CM} \neq 0$

a_{CM} - the common-mode gain

The Common-Mode Rejection Ratio (CMRR)

CMRR describes the ability of a differential amplifier to reject the signals common to both inputs, and to amplify only the difference between the inputs.

$$CMRR = \frac{a_D}{a_{CM}} = \frac{\frac{v_o}{u_D}}{\frac{v_o}{v_{CM}}} = \frac{v_{CM}}{u_D}$$

$$CMRR(dB) = 20 \lg \frac{a_D}{a_{CM}}$$


Ideally $a_{CM} \rightarrow 0 \Rightarrow CMRR \rightarrow \infty$

Really $CMRR = 100 \div 120 dB$

Real op-amps (like the 741) have CMRR of ~90 dB, meaning the ratio of gains is 30000.


Electromyography
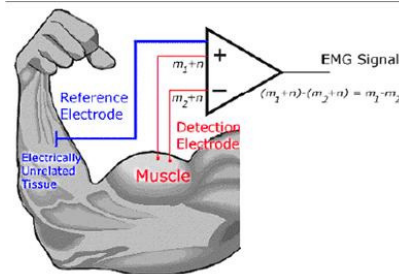
<https://www.youtube.com/watch?v=gHsZ0bwXMsg>



The frequency response of the op-amps

- Really a_D has a finite value and it's function of frequency.
- The **frequency response** of any circuit is the graph of the magnitude of the gain in decibels (dB) as a function of the frequency of the input signal.
- The frequency response of an op-amp is a **low pass filter characteristic**.
- The bandwidth (B) is the frequency at which the power of the output signal is reduced to **half** that of the maximum output power. This occurs when the gain drops by **3 dB**.

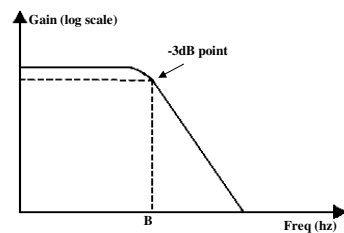


$$10\lg\left(\frac{1}{2}\right) = -3.0103\text{dB} \quad \rightarrow \text{power}$$

$$20\lg\left(\frac{1}{\sqrt{2}}\right) = 20\lg(0.707) = -3.0103\text{dB} \quad \rightarrow \text{voltage}$$

Ideal OA versus real OA

Parameter	Ideal Operational Amplifier	Typical Operational Amplifier
Differential voltage gain a_D	∞	10^5 - 10^9
Common mode voltage gain	0	10^{-5}
Gain bandwidth product f	∞	1-20 MHz
Input resistance R	∞	$10^6\Omega$ (bipolar) 10^9 - $10^{12}\Omega$ (FET)
Output resistance	0	100-1000 Ω

The transfer characteristic of an op-amp

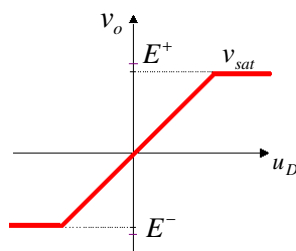

Saturation means that the output voltage clips at some maximum value V_{sat} , typically a couple of volts lower than the positive supply voltage E^+_{supply} .

Application. Saturation

Given: The gain of an op-amp (in open loop) is 1 million ($a_D = 10^6$). The high supply voltage E^+_{supply} is 15 V. The op-amp saturates at 13 V.

To do: Calculate the input voltage difference v_D that will cause saturation.



Solution:

$$v_D = \frac{v_0}{a_D} = \frac{13V}{10^6} = 13\mu V$$


With only 13 μV of differential input, the op-amp is **already saturated!**

- Because of their very high open loop gain, OAs are almost exclusively used with some additional circuitry (mostly with resistors and capacitors), required to ensure a **negative feedback loop**.
- The negative feedback stabilizes the output within the operational range and provides a much smaller but precisely controlled gain, the so-called **closed loop gain**.

The Open-loop op-amp → The Comparator

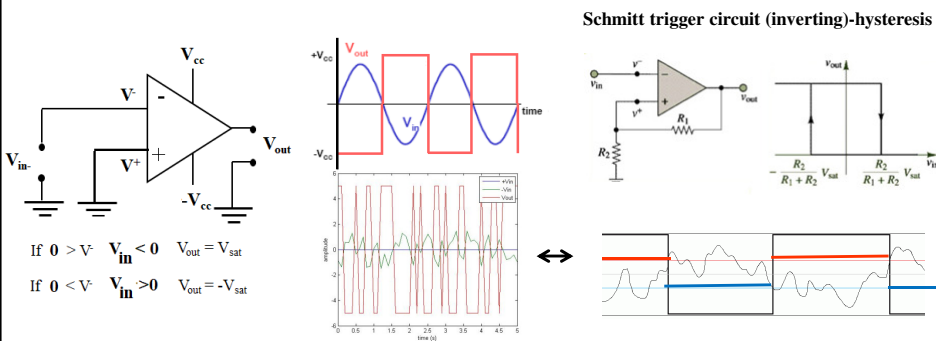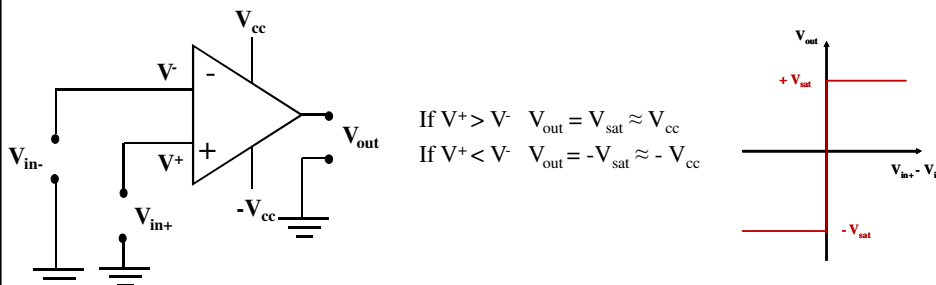

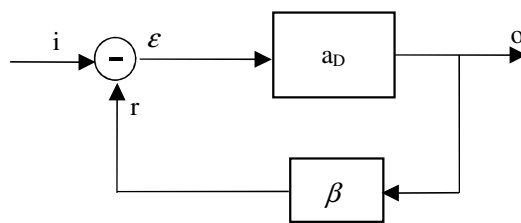The Closed-loop op-amp. The negative feedback



$$o = a_D \varepsilon$$

$$r = \beta \cdot o$$

$$\varepsilon = i - r = i - \beta \cdot o$$

$$A = \frac{o}{i} = \frac{a_D \varepsilon}{i} = \frac{a_D (i - \beta \cdot o)}{i}$$

$$A = a_D (1 - \beta \cdot A) \Rightarrow$$

$$A = \frac{a_D}{1 + \beta \cdot a_D}$$

For a *high* a_D it results $\beta a_D \gg 1$ and finally:

$$A = \frac{a_D}{\beta \cdot a_D} = \frac{1}{\beta}$$


The gain is **independent** of a_D and the circuit is **very stable**.

Basic Operational Amplifier Circuits

There are a lot of circuits with OAs performing various mathematical operations. The transfer characteristic can be derived applying **Kirchhoff's rules** and the following assumptions (Op-amp is considered **ideal**):

$$v^+ = v^-; i^+ = i^-$$

The inverting amplifier

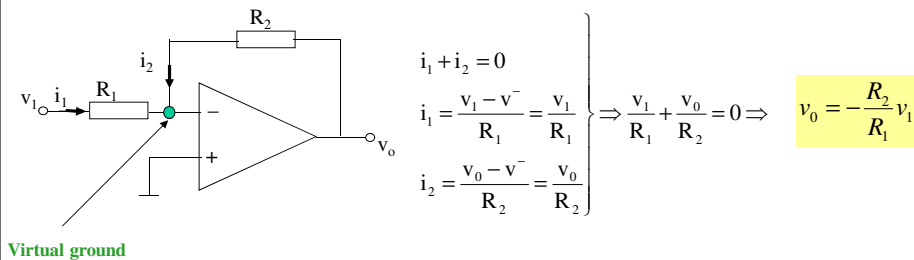


The inverting voltage follower


$$\text{If } R_1 = R_2 \Rightarrow A = -1 \quad v_0 = -v_i$$

The summing amplifier

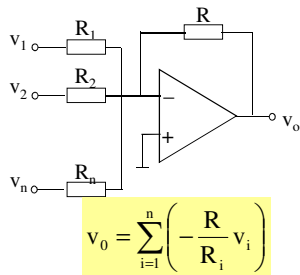It's a logical extension of the inverting amplifier circuit, with two or more inputs.




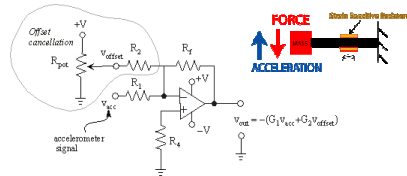Application: adjusting d.c. offset in a **piezoresistive accelerometer** signal
<https://www.youtube.com/watch?v=ykBn4IxStrU>



Piezoresistive strain gauges - semiconductor material - changes in resistance when the material stretched or compressed. They have a much higher gauge factor than bonded foil strain gauges.


The noninverting amplifier

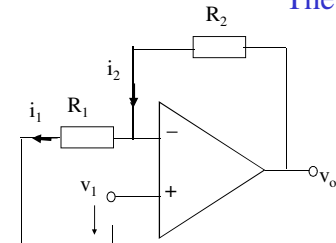

$$\left. \begin{aligned} i_1 &= i_2 \\ i_1 &= \frac{v_1 - 0}{R_1} = \frac{v_1}{R_1} \\ i_2 &= \frac{v_0 - v^-}{R_2} = \frac{v_0 - v_1}{R_2} \end{aligned} \right\} \Rightarrow \frac{v_1}{R_1} = \frac{v_0 - v_1}{R_2} \Rightarrow v_0 = \left(1 + \frac{R_2}{R_1} \right) v_1$$

$$v_0 = \left(1 + \frac{R_2}{R_1} \right) v_1$$


The follower

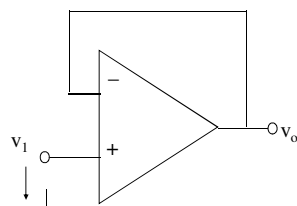

$$\begin{aligned} v_0 &= v_1 \\ A &= 1 \end{aligned}$$

- This configuration is very important when the input signal needs **to be isolated** from the output.
- It has a very low output impedance that is very useful in some **impedance-matching applications**.

Differentiator circuit

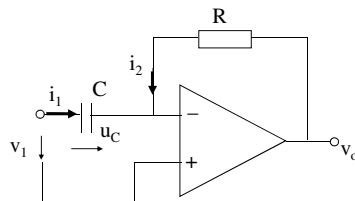


$$\begin{aligned} i_1 + i_2 &= 0 \\ i_1 &= C \frac{dv_1}{dt}; \quad i_2 = \frac{v_0}{R} \\ C \frac{dv_1}{dt} + \frac{v_0}{R} &= 0 \end{aligned}$$

$$v_0 = -RC \frac{dv_1}{dt}$$


Applications include the rate-of-change indicators for process instrumentation.

- monitoring (or controlling) the rate of **temperature** change in a furnace, where too high or too low of a temperature rise rate could be detrimental. V_{out} could be used to drive a comparator, which would signal an alarm or activate a control if the rate of change exceeded a preset level.

The integrator

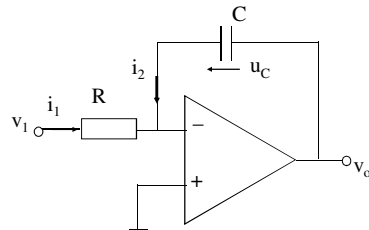

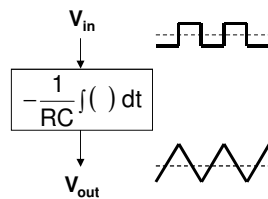
$$\left. \begin{aligned}
 i_1 + i_2 &= 0 \\
 i_1 &= \frac{v_1 - 0}{R} = \frac{v_1}{R} \\
 i_2 &= \frac{dq}{dt} = \frac{d(Cu_c)}{dt} = C \frac{du_c}{dt} \\
 u_c &= v_0 - 0 = v_0 \Rightarrow \\
 i_2 &= C \frac{dv_0}{dt} \\
 \frac{v_1}{R} + C \frac{dv_0}{dt} &= 0
 \end{aligned} \right\} \Rightarrow v_0 = -\frac{1}{RC} \int v_1 dt$$



Application: totalizer in the industrial instrumentation trade
-to integrate a signal representing water flow, producing a signal representing total quantity of water that has passed by the flowmeter.

Difference amplifier

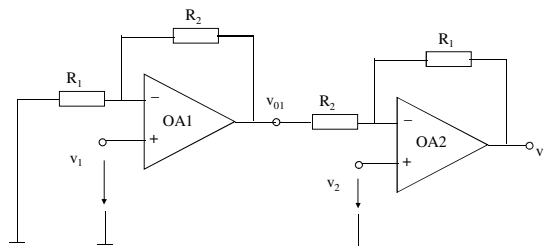

$$v_{01} = \left(1 + \frac{R_2}{R_1}\right)v_1$$


$$v'_0 = -\frac{R_1}{R_2}v_{01} = -\frac{R_1}{R_2}\left(1 + \frac{R_2}{R_1}\right)v_1 = -\left(1 + \frac{R_1}{R_2}\right)v_1$$


$$v''_0 = \left(1 + \frac{R_1}{R_2}\right)v_2 \xrightarrow{\text{Using the overlapping principle}} v_0 = v'_0 + v''_0 = \left(1 + \frac{R_1}{R_2}\right)(v_2 - v_1)$$

Instrumentation amplifiers

- The **instrumentation amplifier** amplifies the difference between two input signals (-) and (+). It has the next essential characteristics:
 - High input impedance
 - Low output impedance
 - Low offset
 - High linearity
 - Stable gain
 - ability to reject common-mode inputs (CMRR)
- **Instrumentation amplifier** → interface sensors into the electronics package → noises, ground-voltages differences = common-mode voltages.
- **Instrumentation amplifier** → **VERY HIGH CMRR**

ONE-op-amp Instrumentation Amplifier

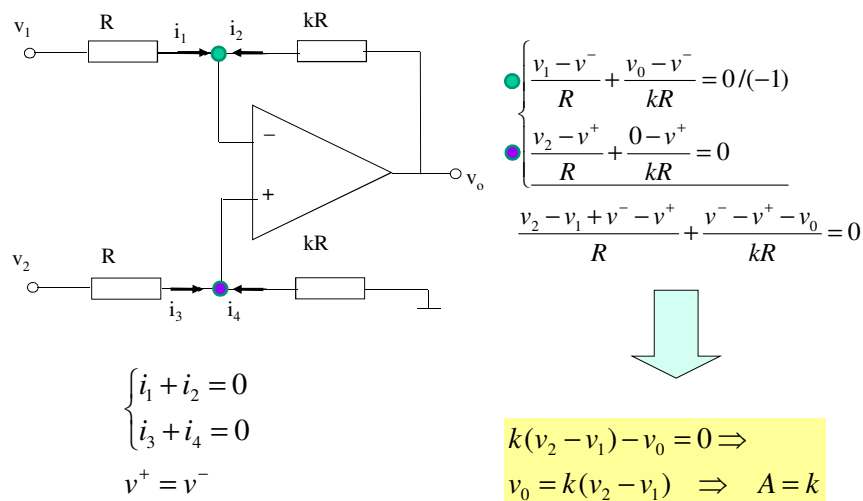

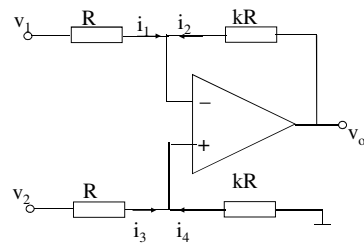


When external feedback resistors are used with OA → resistor-mismatch errors → **low CMRR**

Solution: one-op-amp instrumentation amplifier realized in **integrated** technology (IC).

It can be demonstrated that:

$$CMRR_{IA} = CMRR_{OA}$$

THREE-op-amp Instrumentation Amplifier

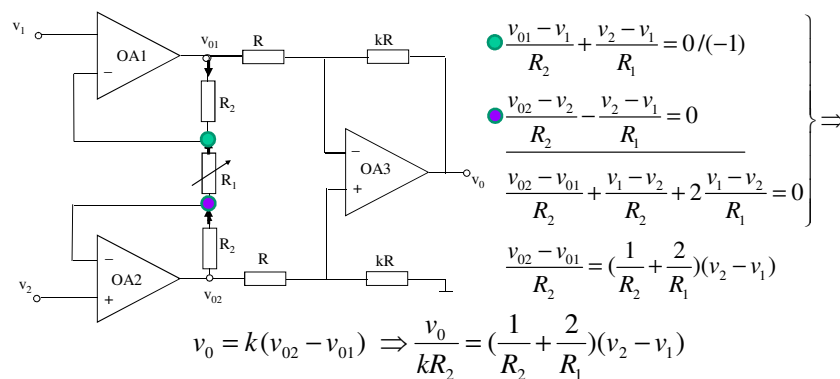


$$v_0 = k\left(1 + 2\frac{R_2}{R_1}\right)(v_2 - v_1)$$

$$CMRR_{AI} = \left(1 + 2\frac{R_2}{R_1}\right)CMRR_{AO3}$$


<https://www.youtube.com/watch?v=c2rW4EPuXyw>

Bionic eye video

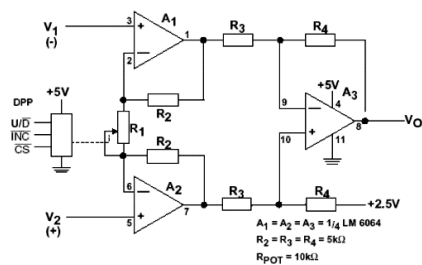
In multiplexed systems → Programmable gain IA → R_1 is a digitally programmed potentiometer



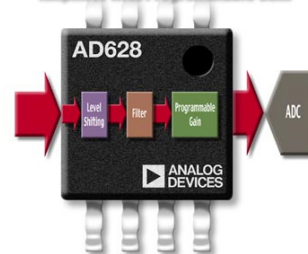First High Common-Mode Differential Amplifier with Programmable Gain




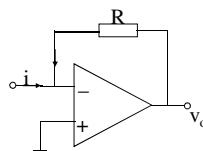CURRENT measurement (relative to ground) CURRENT TO VOLTAGE CONVERTOR




$$i + \frac{v_0 - 0}{R} = 0 \quad v_0 = -Ri$$

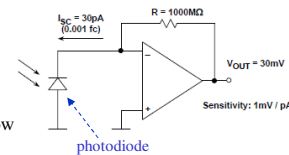This is a very useful device when sensing with very low impedance sensors (thermocouple or photodiode)



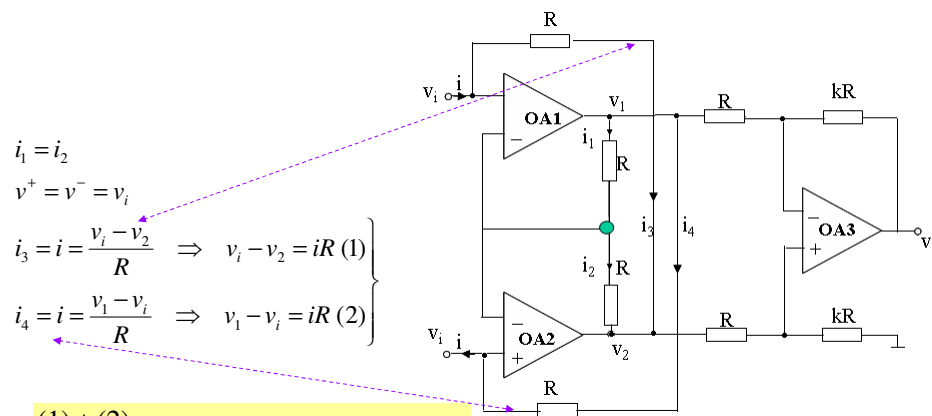CURRENT measurement (floating) CURRENT TO VOLTAGE CONVERTOR






$$\left. \begin{aligned} i_1 &= i_2 \\ v^+ &= v^- = v_i \\ i_3 &= i = \frac{v_i - v_2}{R} \Rightarrow v_i - v_2 = iR \quad (1) \\ i_4 &= i = \frac{v_1 - v_i}{R} \Rightarrow v_1 - v_i = iR \quad (2) \end{aligned} \right\}$$

(1) + (2):

$$v_i - v_2 + v_1 - v_i = 2Ri \Rightarrow v_2 - v_1 = -2Ri$$

$$v_0 = k(v_2 - v_1) = -2kRi$$


Resistance to voltage converter

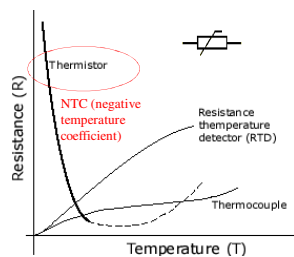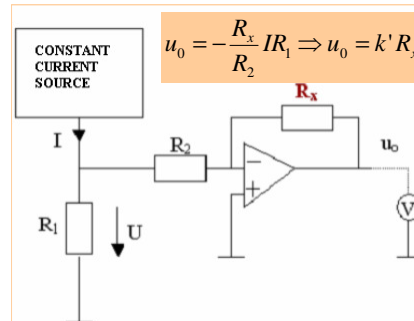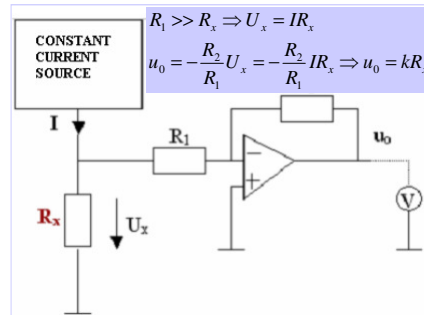

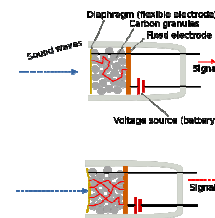
Example of sensors associated with resistance to voltage converters:

-thermistors which change resistance as a function of the temperature

-carbon microphones which alter their resistance in response to the changing in acoustical pressure



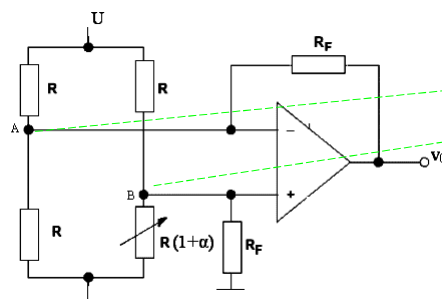Single op-amp bridge amplifier for single-element varying bridge



$$R + dR = R(1 + dR/R) = R(1 + \alpha)$$

$$v_A = \frac{U}{2}; \quad v_B = \frac{1 + \alpha}{2 + \alpha} U$$

$$(+) \quad \frac{v_B - U}{R} + \frac{v_B - 0}{R(1 + \alpha)} + \frac{v_B - 0}{R_F} = 0$$

$$(-) \quad \frac{v_A - U}{R} + \frac{v_A - 0}{R} + \frac{v_A - v_0}{R_F} = 0$$

It results:


$$v_0 = \frac{U}{2} \frac{R_F}{R(1 + \frac{R}{2R_F})} \frac{\alpha}{1 + \alpha}$$

-poor gain accuracy

-low CMRR

-The output is nonlinear

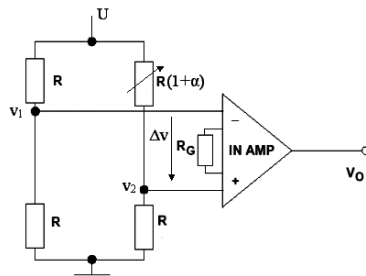Instrumentation amplifier for single-element varying bridge



$$v_0 = A \Delta v$$


$$\Delta v = v_1 - v_2 = \frac{U}{2} - \frac{U}{\alpha + 2}$$

$$v_0 = A \cdot U \frac{\alpha}{4(1 + \frac{\alpha}{2})} \approx AU \frac{\alpha}{4} \quad \alpha \ll 1$$

Linear response

- Better gain accuracy (by adjusting R_G)
- high CMRR (due to AI)
- The output is nonlinear (can be corrected by a software procedure)

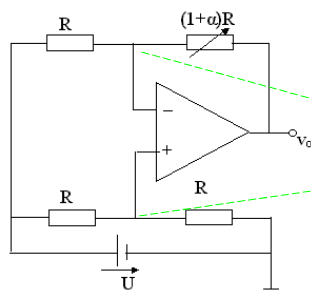Active bridge- linear bridge- hardware procedure



$$v^+ = \frac{U}{2} = v^-$$

$$\left. \begin{aligned} \frac{U - v^-}{R} + \frac{v_0 - v^-}{R(1 + \alpha)} &= 0 \\ \frac{U - v^+}{R} + \frac{0 - v^+}{R} &= 0 \cdot (-1) \\ \frac{v^+ - v^-}{R} + \frac{v_0 - v^-}{R(1 + \alpha)} + \frac{v^+}{R} &= 0 \end{aligned} \right\} \Rightarrow v_0 = -\alpha \frac{U}{2}$$

- The response is linear for every value of α
- Because the output voltage is a small one, this will be amplified with a second amplifier circuit

Power amplifiers

$$P_o = P_i A_p \quad [\text{W}]$$

output input · power gain

Linear DC Motors, Voice Coil Motors (VCM) or Voice Coil Actuators (VCA) consist of two separate parts: the magnetic housing and the coil. A current carrying conductor placed in a magnetic field will have a force applied upon it.
https://www.youtube.com/watch?v=PT42TQ9_LEw


They are used in driving actuators:

- audio amplifiers: used to *drive speakers* and *voice coil actuators*
- amplifiers for *solenoid actuators* and *motors*.

Power amplifiers: *linear amplifiers & pulse modulated amplifiers*



Class A power amplifier-LINEAR

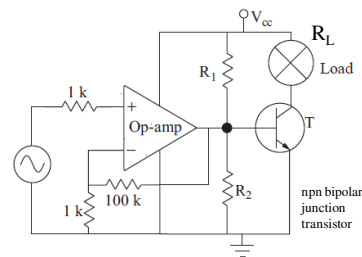- The amplifier is set for a gain of 101 (noninverting amplifier).
- The output drives the transistor, whose output will swing, at most between 0 and V_{cc} , and supplies a current that is V_{cc}/R_L .
- The transistor may be viewed as a current amplifier since its collector current is the base current multiplied by the amplification of the transistor




Pulse Width Modulated (PWM) Amplifiers

- **Control the power** supplied to a load by controlling how long the load is connected to the power (pulse width) rather than by controlling the amplitude.
- **Triangular wave frequency** must be much higher than the signal being represented.
 - Example: if this is used to dim a lightbulb using a 60Hz source, the PWM must be on the order of 10–20 times that (i.e., 600–1200 Hz) to properly represent the signal

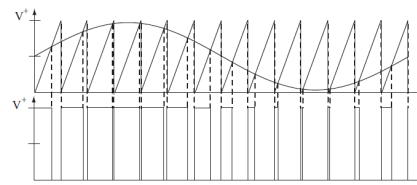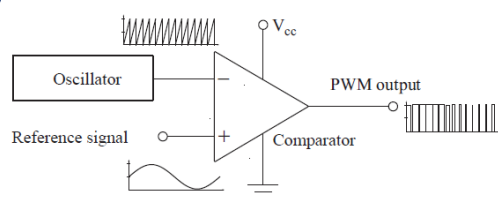

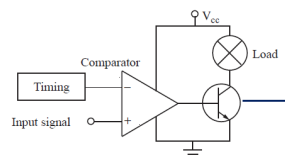The sinusoidal signal's amplitude is represented as pulse widths.





→ A load driven by a PWM circuit.

→ The transistor serves as a switch
 The power is controlled by the average of the PWM signal.

Speed control of a DC motor

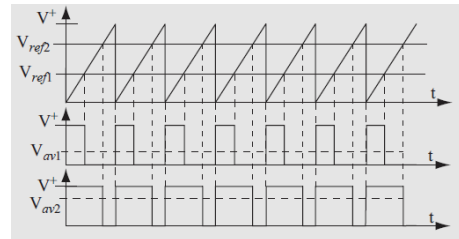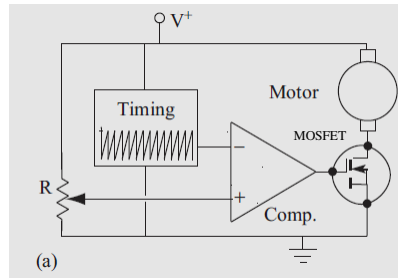The speed is proportional to the average voltage across the motor



- The speed control potentiometer
- The PWM generator

The generation of PWM signals for two positions of the potentiometer.

<https://www.youtube.com/watch?v=K-TaJooK6sM>

156




- Consider a case in which you need to extract a 5 mV sine wave from a white noise signal with 5 V amplitude. Are those measurements even possible?
- The answer is **YES!**


Lock-in amplifiers

The phase-sensitive detectors

- Lock-in amplifiers are used to detect and measure **very small AC signals** (few nV).
- Accurate measurements may be made even when the small signal is obscured by **noise sources** many thousands of times larger.
- Lock-in amplifiers use a technique known as **phase-sensitive detection**: the useful signal depends on the phase difference between it and a **reference signal with the same frequency** or a frequency very close to that of useful signal.
- Noise signals, at frequencies other than the reference frequency, are rejected and do not affect the measurement.
- Measured signal is greater as the phase difference between the two signals is less, becoming **maximum when the signals are in phase**.

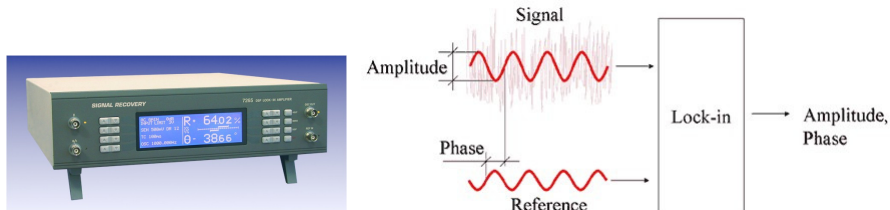


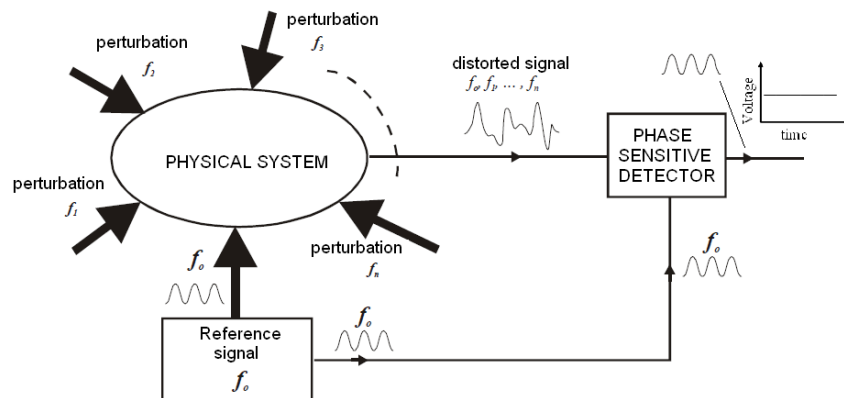The principle of phase-sensitive detectors




- The output signal is **maximum** when the detector input signals are synchronized → **synchronous detection**.
- It acts like a filter-The centre frequency of the filter is locked (hence lock-in)

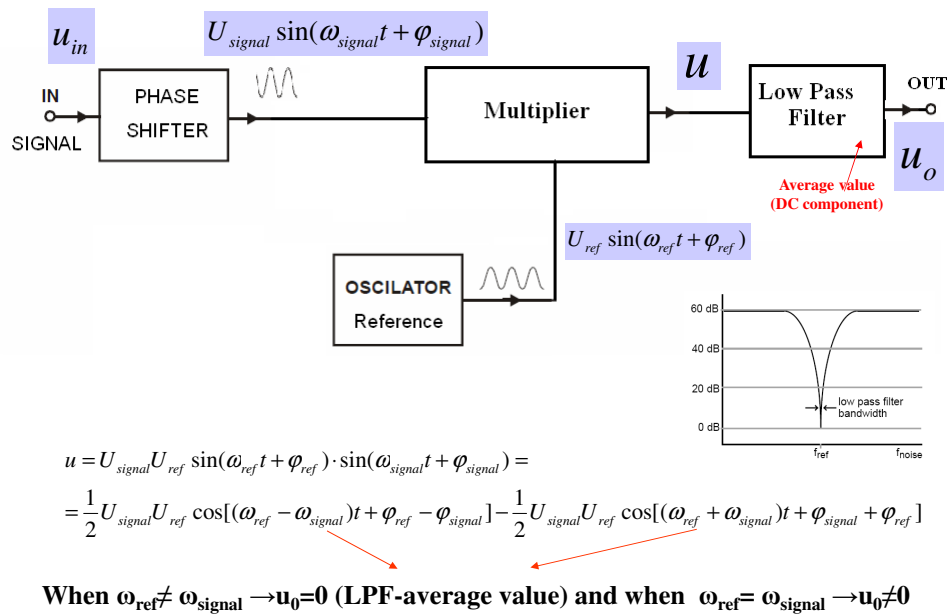The principle of phase-sensitive detectors




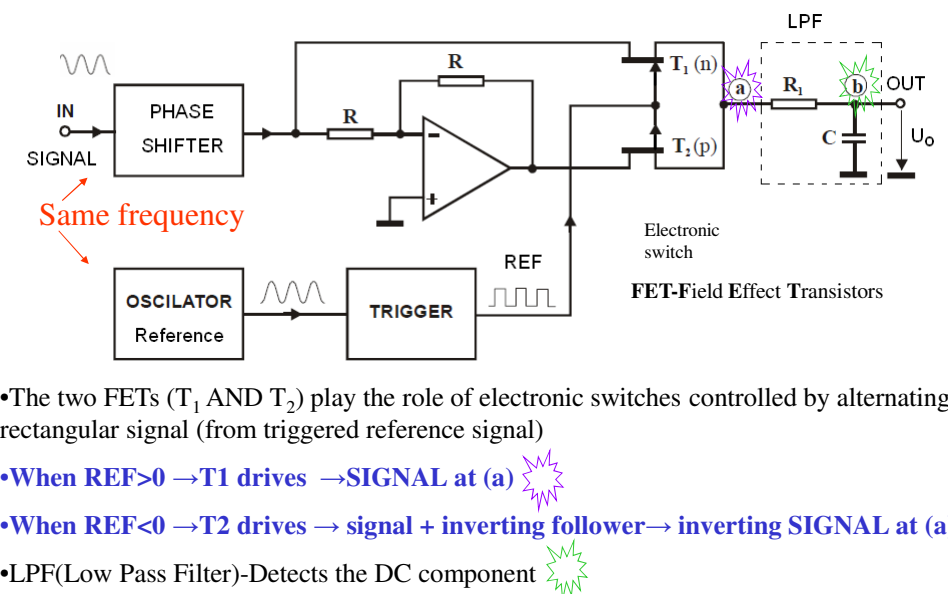
The principle of phase-sensitive detectors




- The two FETs (T_1 AND T_2) play the role of electronic switches controlled by alternating rectangular signal (from triggered reference signal)
- When $REF > 0 \rightarrow T_1$ drives \rightarrow SIGNAL at (a)
- When $REF < 0 \rightarrow T_2$ drives \rightarrow signal + inverting follower \rightarrow inverting SIGNAL at (a)
- LPF (Low Pass Filter) - Detects the DC component

Phase-sensitive detector
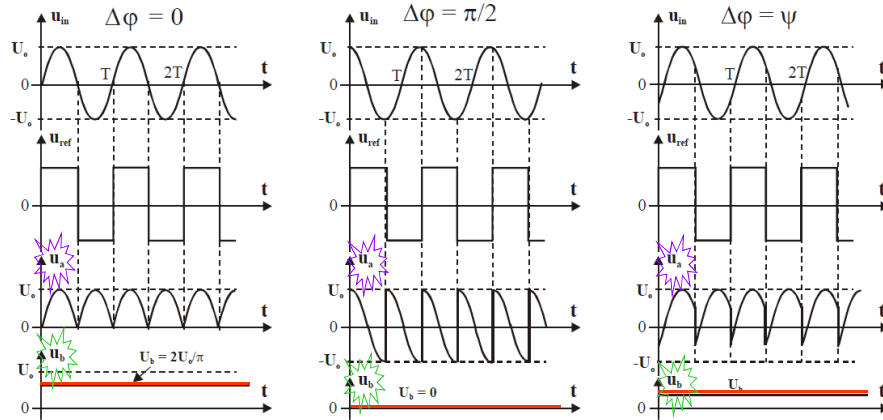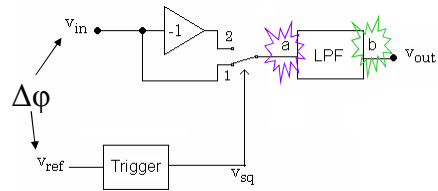
$$u_{in} = U_o \sin(\omega t - \psi) = U_o \sin\left[\omega\left(t - \frac{\psi}{\omega}\right)\right]$$




Phase-sensitive detector

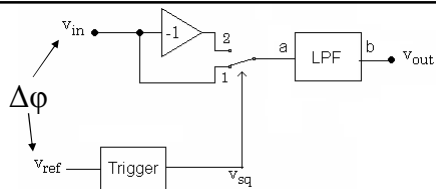

$$u_{in} = U_o \sin(\omega t - \psi) = U_o \sin\left[\omega\left(t - \frac{\psi}{\omega}\right)\right]$$

After the LPF:

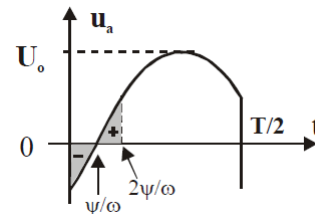

$$U_b = \frac{1}{T} \int_0^{\frac{T}{2}} U_o \sin\left[\omega\left(t - \frac{\psi}{\omega}\right)\right] dt = \frac{2}{T} \int_{\frac{\psi}{\omega}}^{\frac{T}{2}} U_o \sin\left[\omega\left(t - \frac{\psi}{\omega}\right)\right] dt$$

$\tau = t - \frac{\psi}{\omega}$
 Change the variable

$$\longrightarrow U_b = \frac{2}{T} \int_{\frac{\psi}{\omega}}^{\frac{T}{2}} U_o \sin \omega \tau \cdot d\tau \quad \longrightarrow \quad U_b = \frac{2U_o}{\pi} \cos \psi$$

Phase-sensitive detector CONCLUSIONS

$$U_b = \frac{2U_o}{\pi} \cos \psi$$

When $\Delta\phi = \Psi = 0$ (synchronous detection)


$$U_b = \frac{2U_o}{\pi}$$

When $\Psi = 90^\circ$

$$U_b = 0$$

- In the lock-in amplifiers a phase sensitive detector is used as the *selective element*.
- This detector *selects* from the input signal only:
 - these components that have the **same frequency as the reference voltage**.
 - these signals that **are in phase with the reference signal**.
- Noise having a random frequency will be strongly attenuated.
- The phase problems (they appear due to the physical problems, connections, etc) are resolved by the phase shifter.


Lock-in Amplifier (LiA)- applications

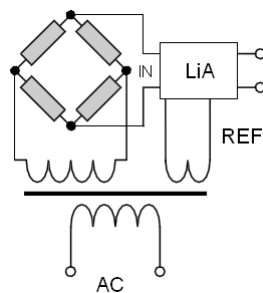

The measurement of **small variations of the resistance** – strain-gauge bridge




From the signal (μV) with noises we can separate only the signal of the frequency the same as supply voltage (bridge= modulator device)

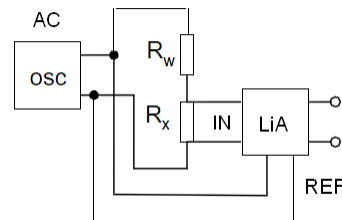The measurement of **small resistances** (micro-ohm-meter) = the measurement of very small voltage drop across the unknown resistance



Lock-in Amplifier (LiA)- applications

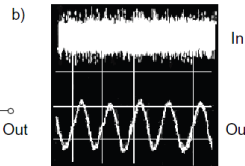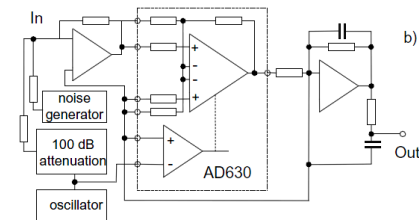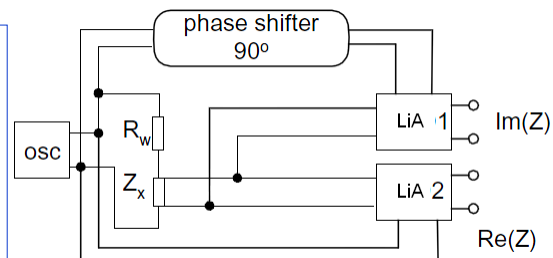- We can separate both components of the vector signal – in phase and shifted by 90° .
- We can analyze the **impedance components $Re(Z)$ and $Im(Z)$** ,
- We can determine the phase shift
- We can perform spectral analysis



Lock-in amplifier
based on the
AD630 device of
Analog Devices